

Design of DTC-Assisted High Performance Fractional-N PLLs

Wanghua Wu

Samsung Semiconductor

2024/11/10

Outline

- **Fractional-N PLL Design Challenges**
- **PLL Architecture Review**
- **DTC-Assisted Phase Detector Design**
- **Digital Calibrations to Enhance PLL Performance**
- **LO Chain Design Example for 5G NR**

Demand for Low Jitter Fractional-N PLLs

Latest wireless standards strive for very high throughput


- WiFi 7 enables 4k-QAM at 7GHz
- Cellular FR2 (MMW) transceivers to support 256-QAM at 40+ GHz

→ RMS jitter <100fs is required for LO

DSB IPN Requirement (dBc)		Integrated RMS jitter (fs) (Int. 1kHz to 100MHz)				
		29.5GHz	40GHz	43GHz	47GHz	7.125GHz
64-QAM	-30	171	126	117	107	707
256-QAM	-33	121	89	83	76	500
1K-QAM	-44	NA	NA	NA	NA	141
4K-QAM	-47	NA	NA	NA	NA	99.8



State-of-the-Art Low Jitter Fractional-N PLLs

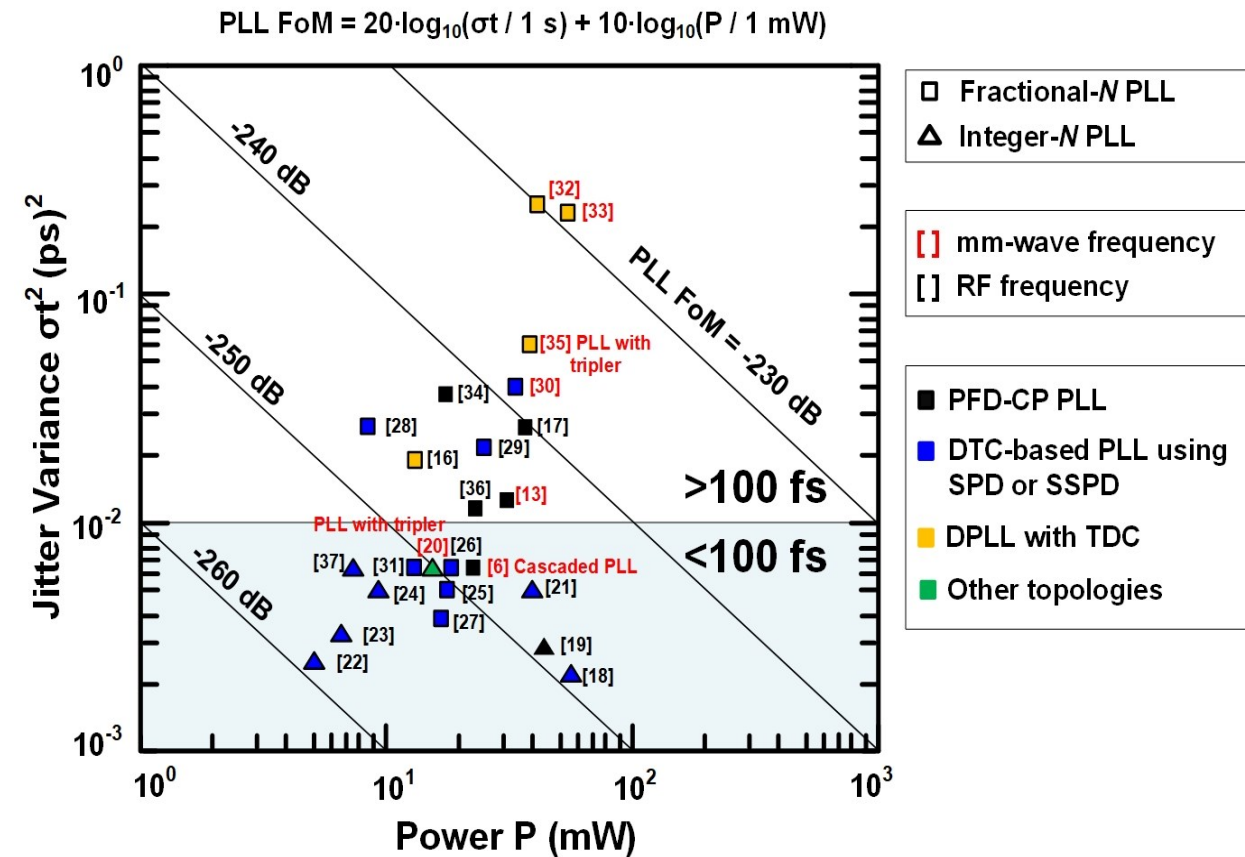- A few frac. N PLLs achieved $<100\text{fs}_{\text{rms}}$ jitter; FoM is still worse than integer-N PLLs
- Even harder for mmW PLLs due to mmW VCO
- Analog/digital PLLs using DTC-assisted PD achieves lower jitter and better FoM




Major Noise Source in Any PLLs

 
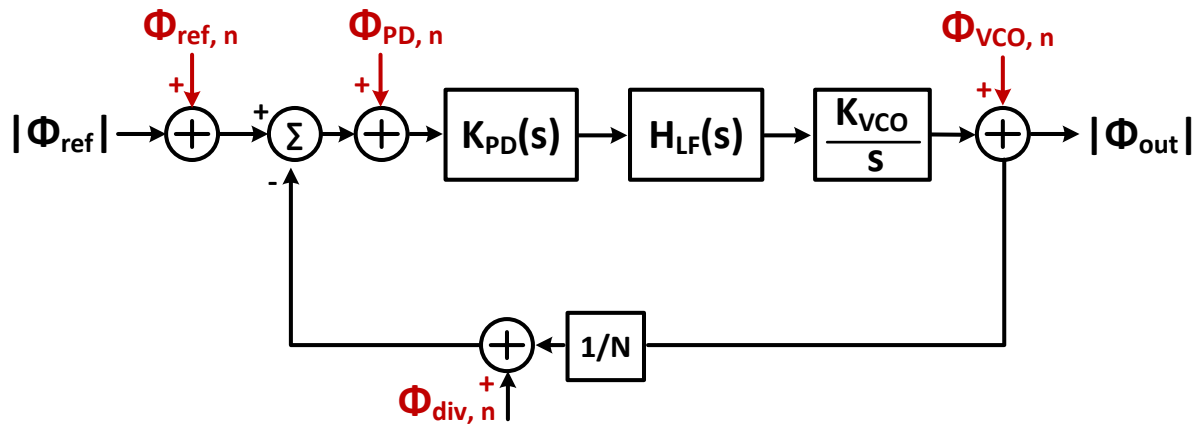
- Major noise source in a PLL
 - VCO/DCO → Dominate
 - CLKREF
 - Phase detector (PD) → try to minimize
 - Feedback divider → negligible



 SSB PN contributors at a low jitter 6-GHz PLL output




Extra Challenges in Fractional-N PLLs

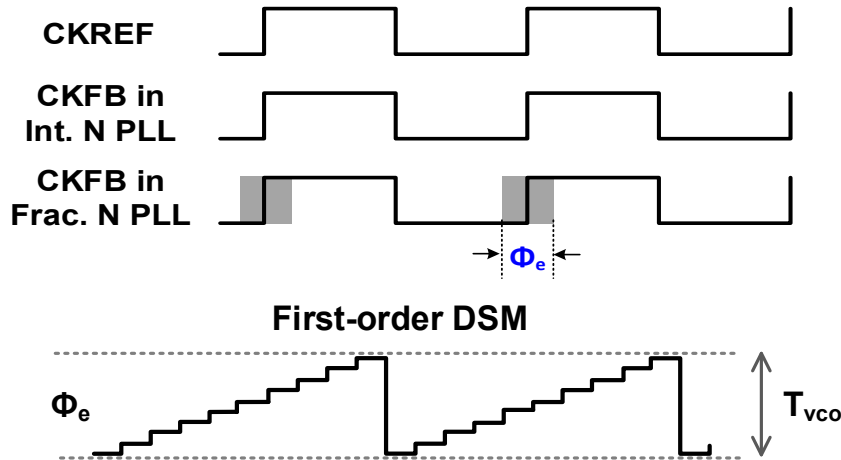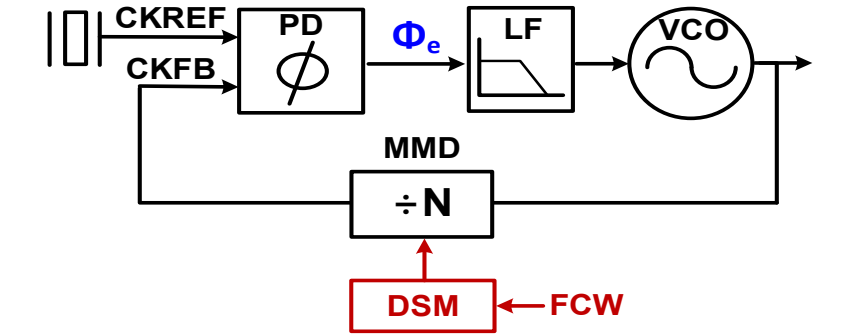


- Mash1:** $-T_{VCO}/2 \leq \Phi_e \leq +T_{VCO}/2$
- Mash1-1:** $-T_{VCO} \leq \Phi_e \leq +T_{VCO}$
- Mash1-1-1:** $-2T_{VCO} \leq \Phi_e \leq +2T_{VCO}$

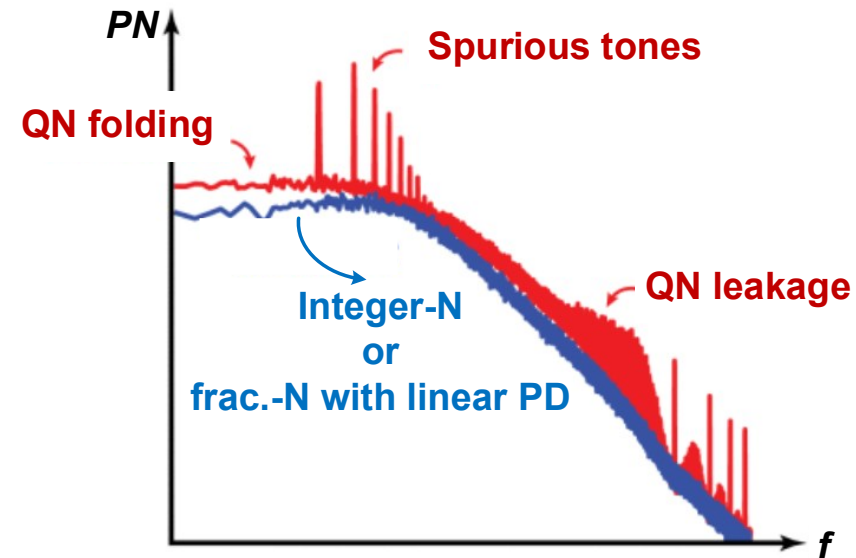- **DSM QN**
- **Much wider dynamic range (DR) needed in PD**
- **Fractional spurs:**
 - **MMD, PD nonlinearity → result in noise folding, higher inband noise**
 - **Coupling between VCO/DCO and PD/CLKREF**




Major PLL Topologies – PD is Key Difference


■ Analog PLL using PFD-CP

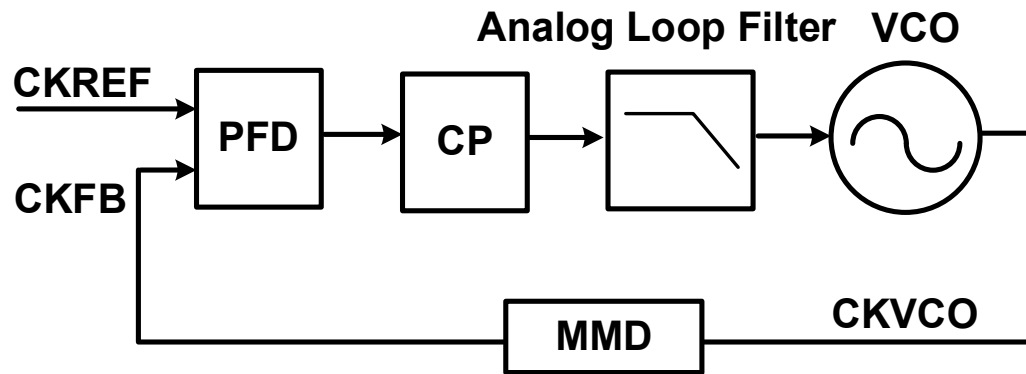

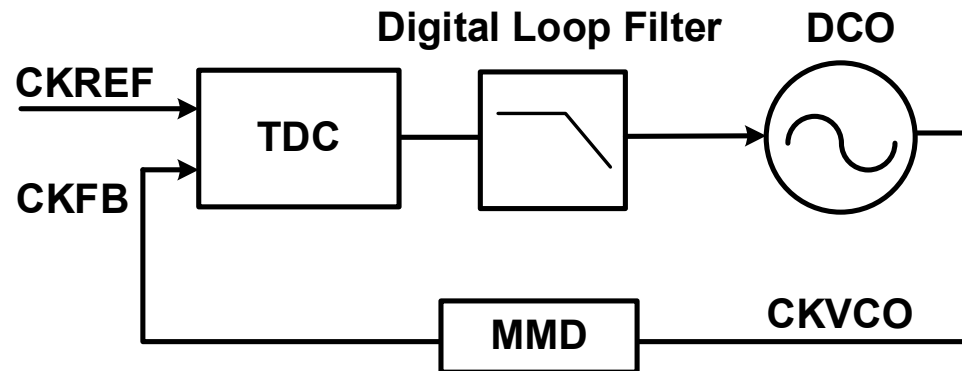■ DPLL using TDC: small LF size, flexible calibration and configurability



■ PLL using DTC-assisted PD

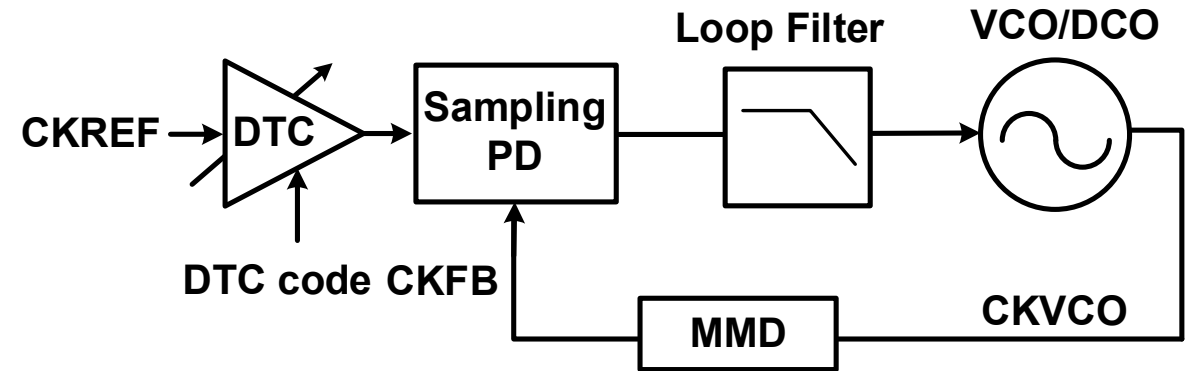


Show more advantages, gain popularity in both academia and industry

PD	▪ Thermal/flicker noise, maybe QN
design	▪ Linearity over required DR
metrics	▪ P_{dc}
	▪ Complexity, area

Outline

- Fractional-N PLL Design Challenges
- **PLL Architecture Review**
- DTC-Assisted Phase Detector Design
- Digital Calibrations to Enhance PLL Performance
- LO Chain Design Example for 5G NR

Advantages of DTC-assisted PD

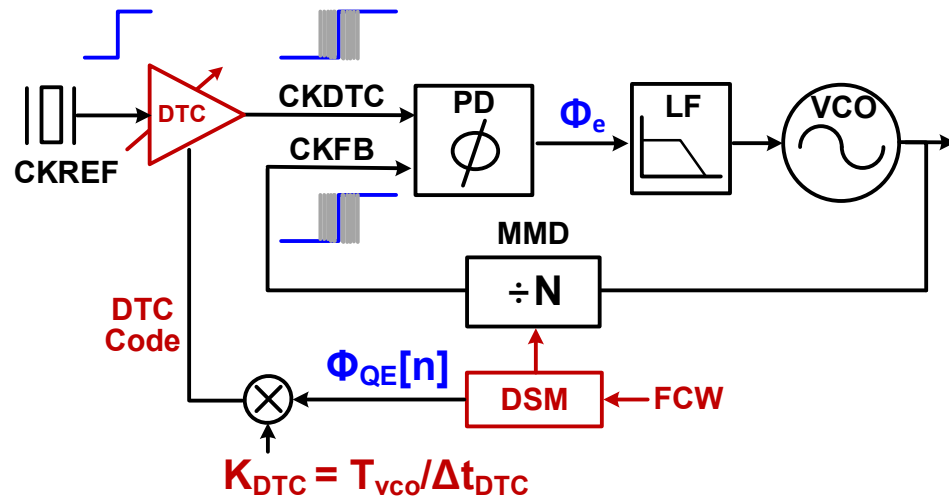


- DTC is a Digital-to-Time Converter
- DTC cancels accumulated QE on CKFB due to DSM

→ Near zero phase error at PD after locking


Just like integer-N case!

 → Can use high gain PD of small dynamic range for lower inband noise, high linearity, lower P_{dc} ...




DTC-based PLL Variations – Digital PLLs

■ DTC-based ADPLL (1st order DSM)

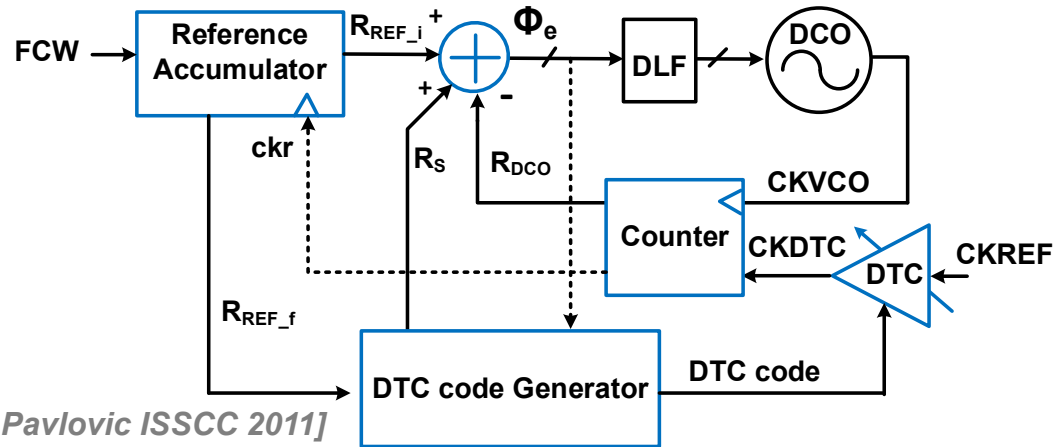


[N. Pavlovic ISSCC 2011]

■ DTC-based Bang-bang PLL

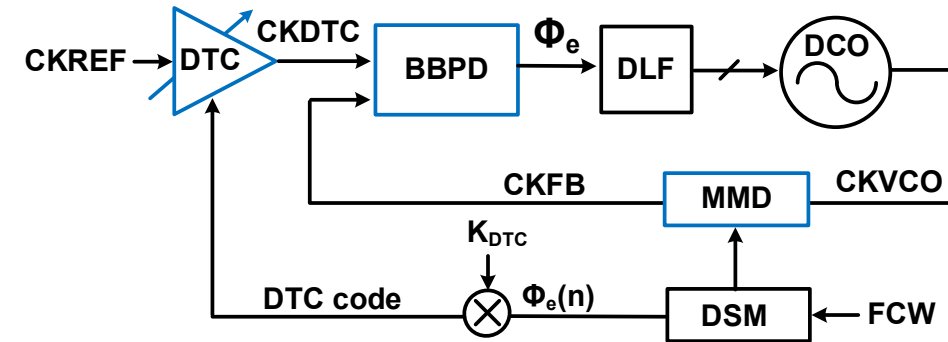

[D. Tasca JSSC Dec. 2011]

■ Digital sampling PLL

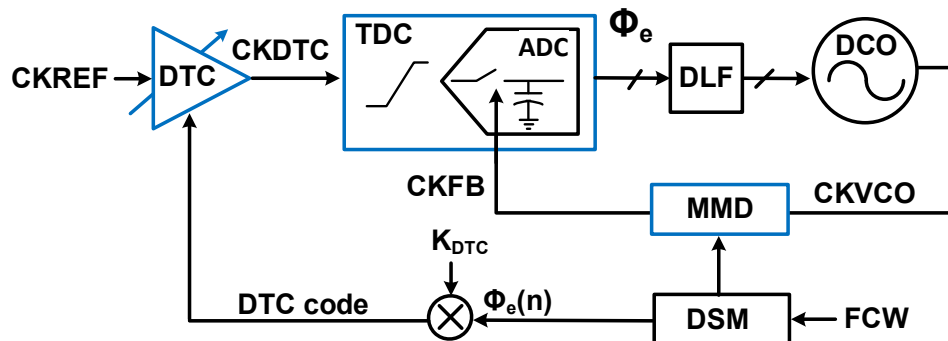


[X. Gao ISSCC 2016]

- Pros:**
- Φ_e is 1- or n-bit digital word
→ Used for LMS based K_{DTC} calibration
 - DLF small chip area
- Cons:**
- BBPD simpler than TDC (sampler+ADC), but need aux circuits to linearize its gain, and achieve fast locking
 - Need DCO


DTC-based PLL Variations – Analog PLLs

■ Analog PLL using sub-sampling PD

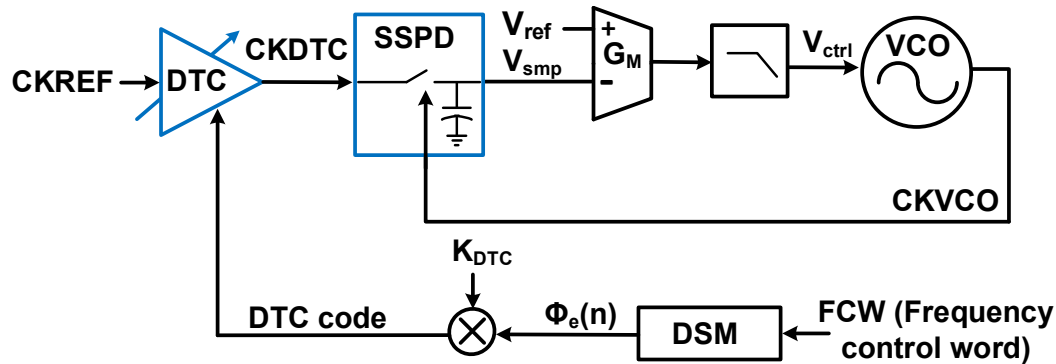

[K. Raczkowski JSSC May 2015]


■ Analog PLL using sampling PD (SPD)

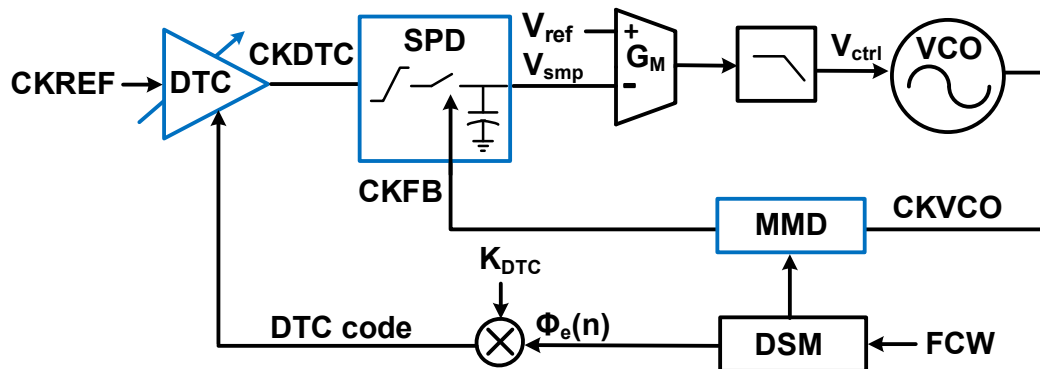

[W. Wu JSSC May 2019]



- Pros:**
- PD is a simple sample-and-hold circuit
 - K_{PD} is linear and well-defined vs. BBPD
 - No high-resolution TDC, no DCO
- Cons:**
- LF C_1 for optimal IPN $\leq 50\text{pF}$ typically (small overhead); type-I removes C_1
 - Need to digitize Φ_e for calibrations

■ DTC-assisted CP PLL

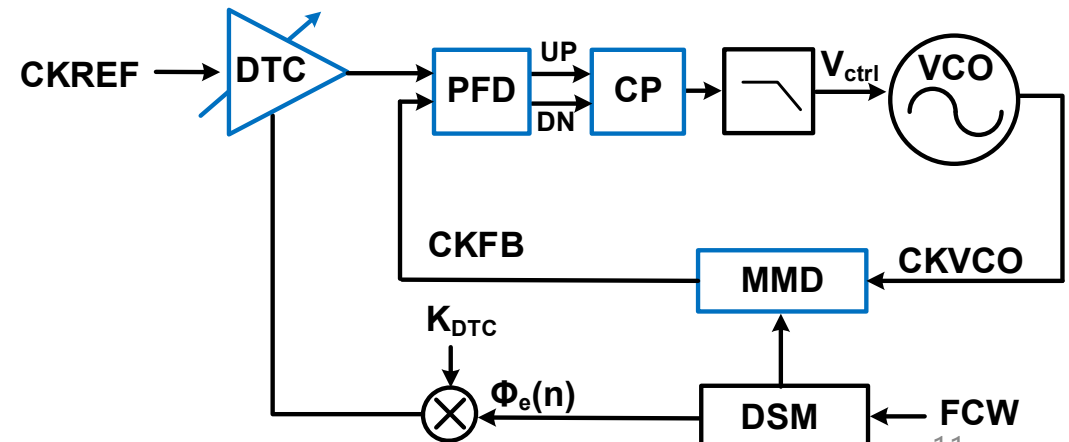

[P. Renukaswamy ISSCC 2023]

DTC vs. TDC as Phase Detector

  

■ TDC-based digital PLL

- In-band noise limited by TDC QN
- $\Delta t \sim 8\text{ps}$ in 14nm CMOS

- Finer $\tau \rightarrow$ Complexity \uparrow
- coarse-fine, Vernier delay line, timing amplifier, noise shaping, stochastic flash TDC, ...

■ DTC-based analog/digital PLL

- QN < other noise
- $\Delta t \sim 100\text{fs}$ in 14nm CMOS

- Broadly applicable

- Bang-bang




- Type-I/II (sub)sampling

- Digital (sub)sampling

Outline

- Fractional-N PLL Design Challenges
- PLL Architecture Review
- **DTC-Assisted Phase Detector Design**
 - **RC Delay Based DTC**
 - **Other DTC Topologies for high linearity**
- Digital Calibrations to Enhance PLL Performance
- LO Chain Design Example for 5G NR

RC Delay Based DTC- Variable Slope DTC

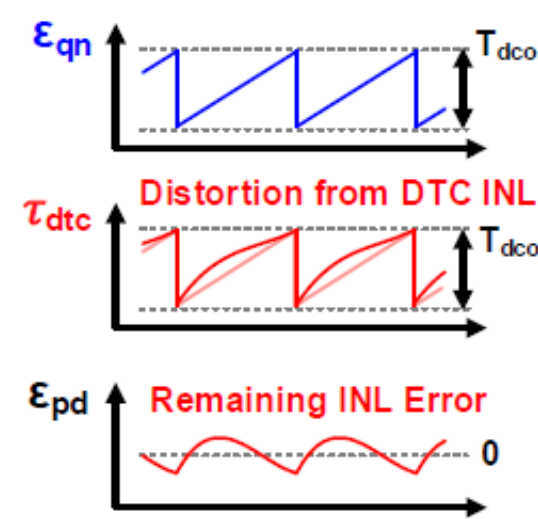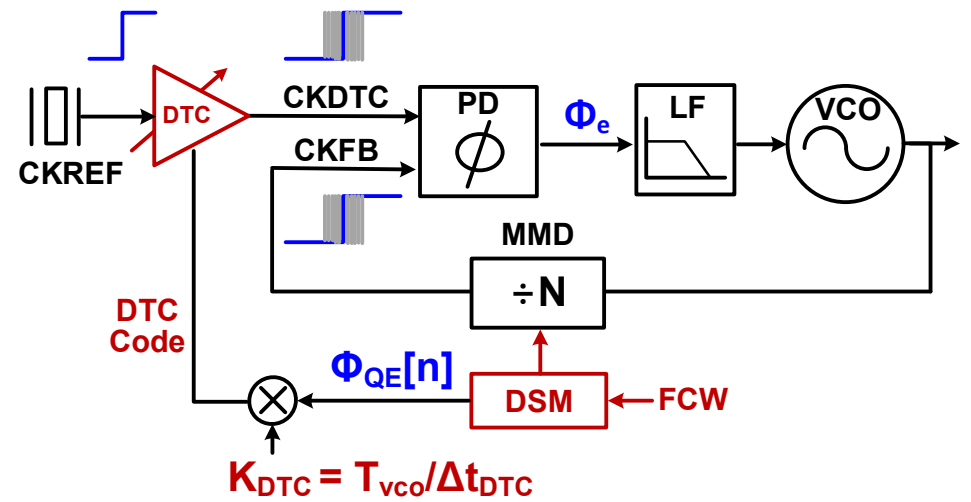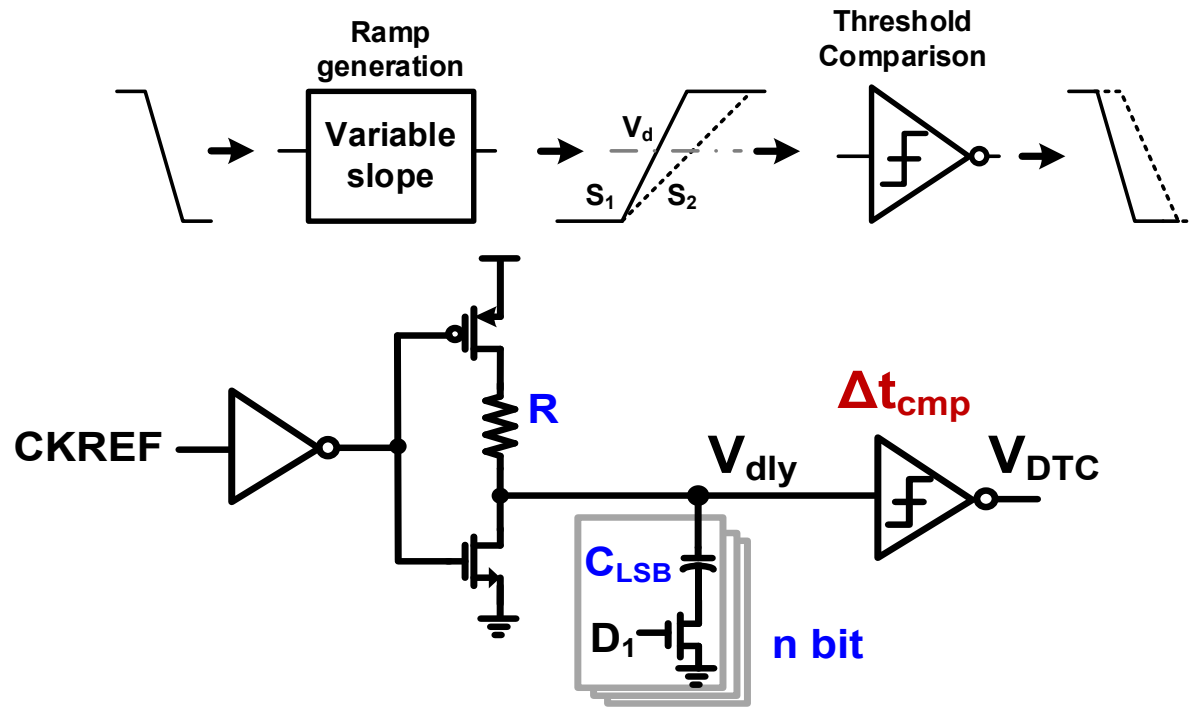

DTC contributes to PLL integrated PN (IPN)

- DTC RMS jitter → inband PN
- DTC quantization noise → inband PN
- DTC nonlinearity → frac. N spurs and noise folding

DTC Noise: Quantization Noise



■ DTC QN

Unit delay $T_{res} = \ln 2 \cdot R \cdot C_{LSB}$

Input referred (at CKREF) $\Phi_{DTC, QN} = \frac{(2\pi \cdot T_{res})^2}{12} \cdot f_{ref}$

e.g., $T_{res} = 400\text{fs}$, $f_{ref} = 104\text{MHz}$, $\rightarrow \Phi_{DTC, QN, \text{ in dBc/Hz}} = -163\text{dBc/Hz}$

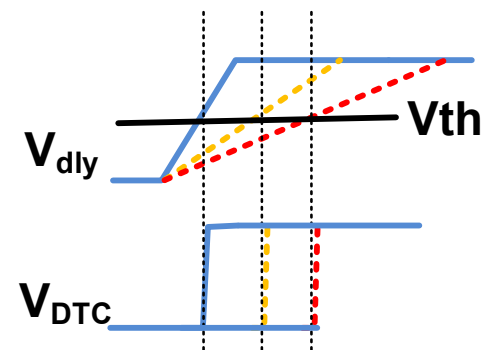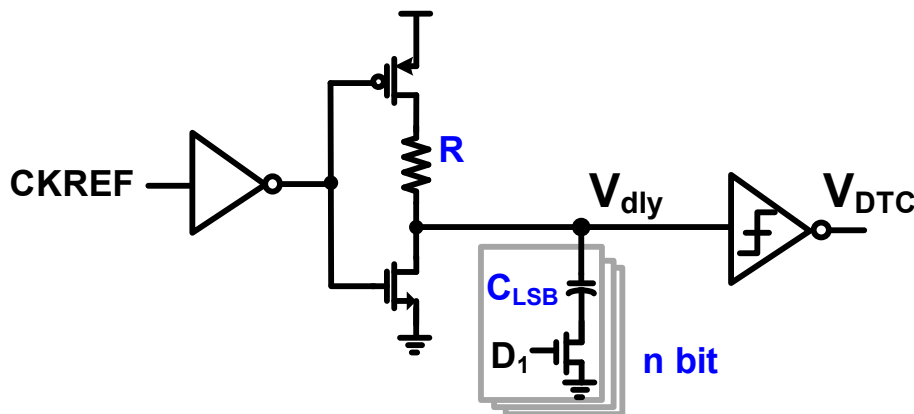10bit \rightarrow total delay range, DR = 400ps, can support 2nd-order DSM with $f_{vco} > 5\text{GHz}$



DTC Noise: Thermal Noise

■ DTC thermal noise: delay stage and INV buffer

1) PN from delay stage:

Depends on slew of V_{dly} , thus, DTC code

SSB PN sampled at half VDD transition considering noise folding is



$$\mathcal{L} \cong 10 \cdot \log_{10} \left[\frac{1}{2} \left(\frac{2\pi \cdot f_{ref}}{k_{slew}} \right)^2 \cdot S_v^{folded}(f_m) \right], k_{slew} = \frac{1}{2RC} \text{ at } \frac{VDD}{2}, S_v^{folded}(f_m) \cong \frac{KT/C}{f_{out}/2}$$

$$\rightarrow \mathcal{L} \cong 10 \cdot \log_{10} \left[2kT \cdot f_{ref} \left(\frac{2\pi}{\ln 2} \right)^2 \cdot \frac{2^n \cdot T_{res}^2}{C_{LSB}} \right] \text{ at mid code,}$$

e.g., C_{LSB} needs $\geq 2fF$ for PN floor $< -171dBc/Hz$



2) PN from INV buffer dominates:

INV BUF size up to hundreds of μm Width

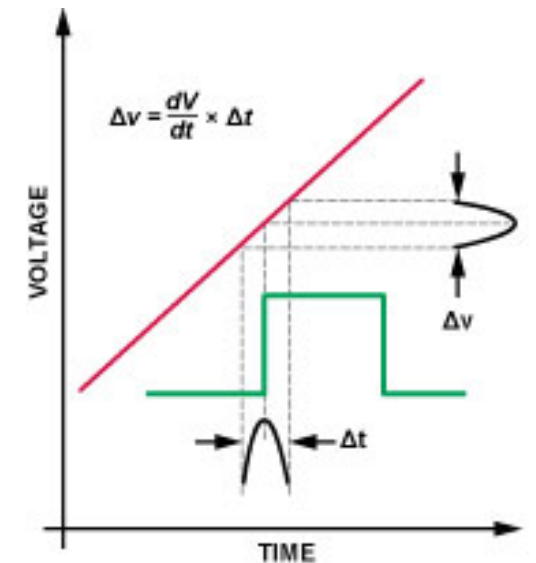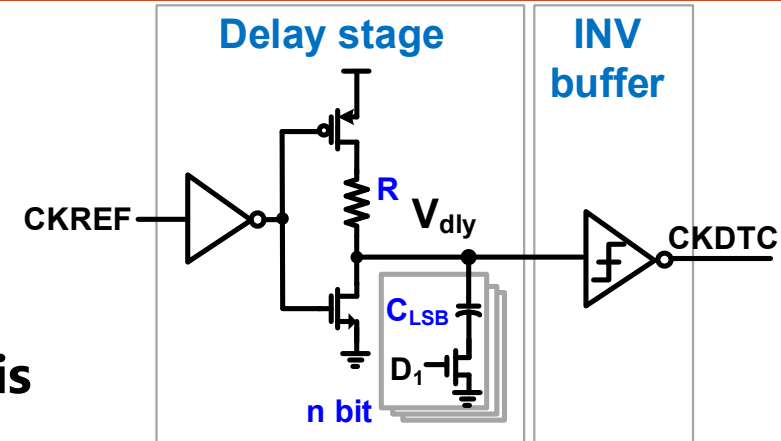

DTC Nonlinearity – Static Distortion

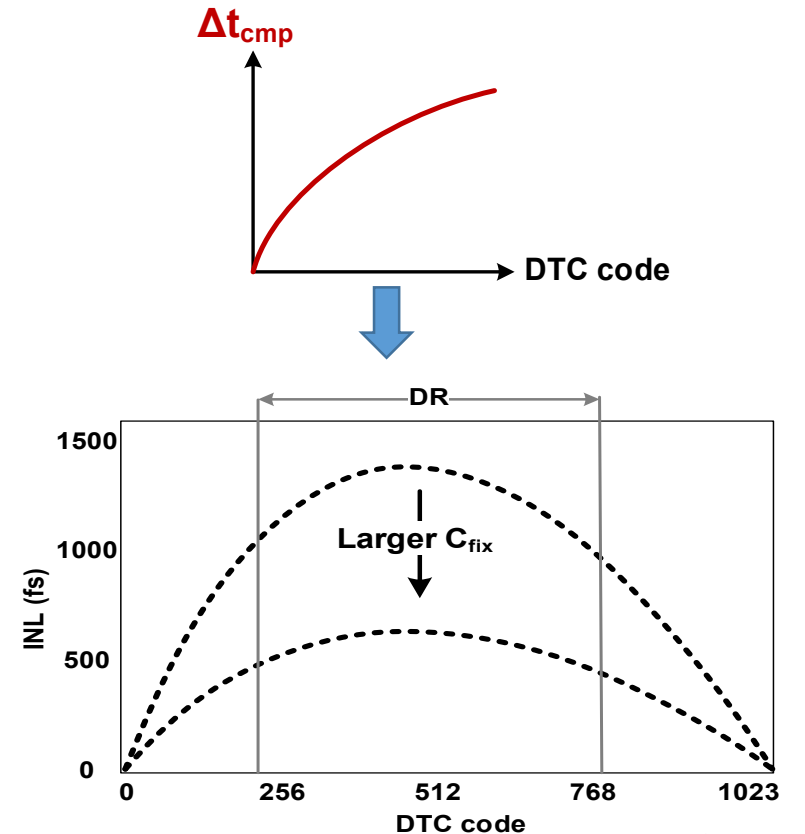
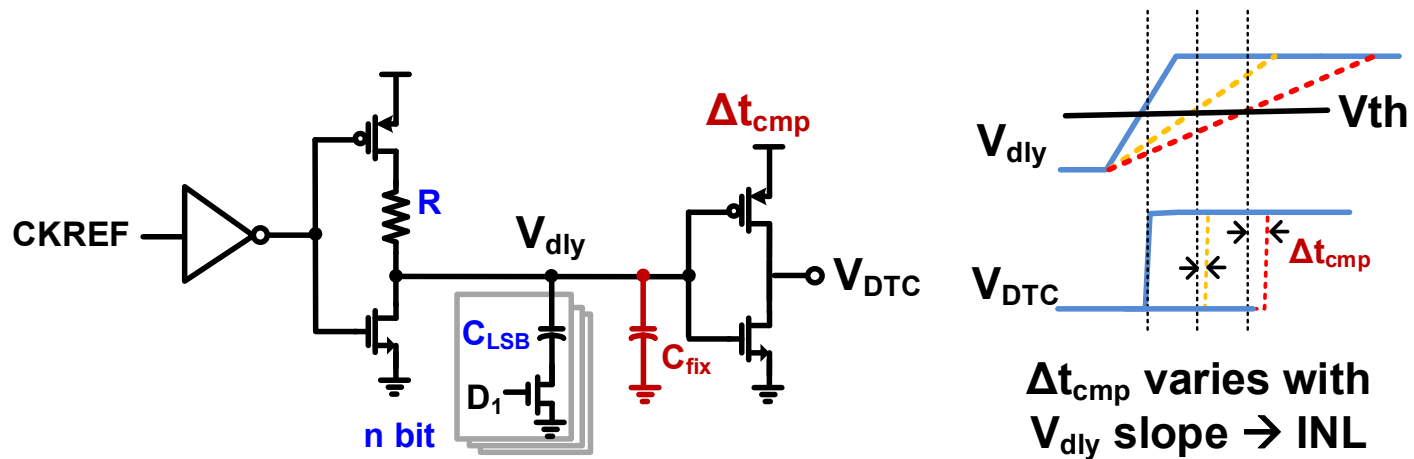
- **Matching of capacitor array** → not dominate as $C_{LSB} \geq 2fF$
- Common centroid layout, DEM to achieve $DNL = \pm 0.2$ LSB for 10bit DTC
- **Code/slope dependent Δt_{cmp}** → **INL, dominate!**
- Fixed cap. (e.g., 1~2 pF) reduces $INL < \sim 2$ LSB
- Parasitic cap of INV BUF serves as fixed cap



DTC Nonlinearity – Dynamic Distortion


- Code-dependent supply settling error → INL, memory effect, dominate!

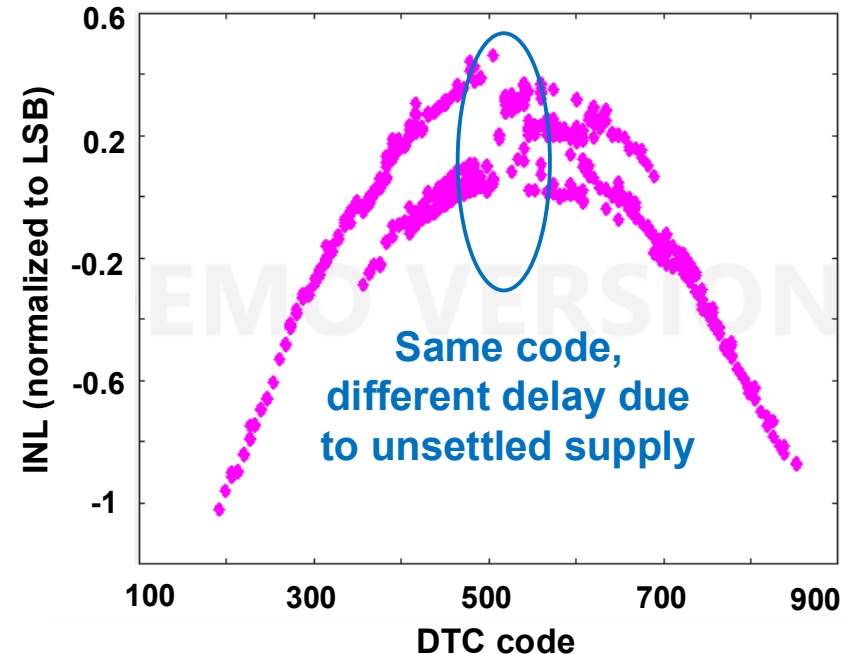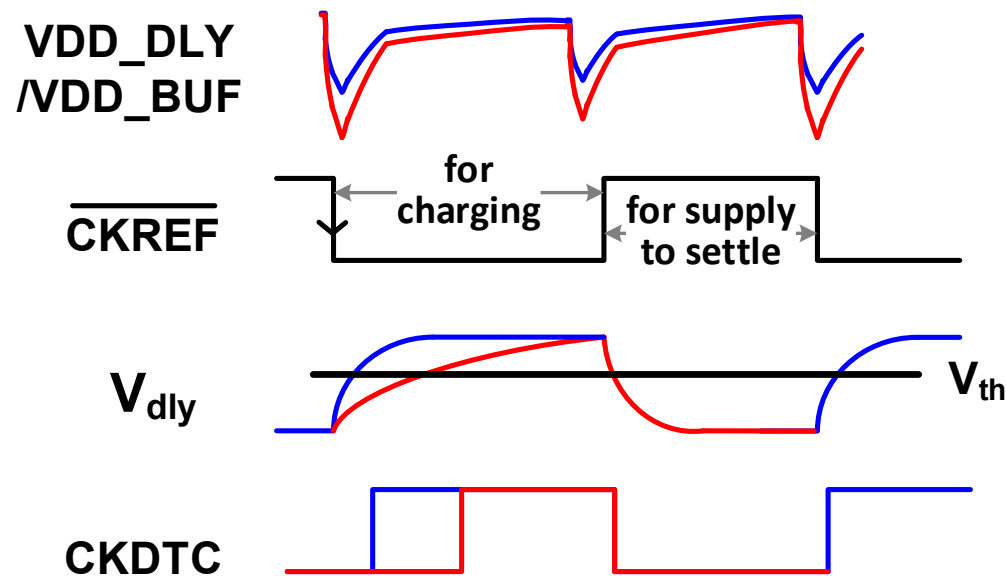Large transient current at CKREF edges, supply dips and resettle each cycle






- Code-dependent charge on bottom plate of unit cap. array
→ INL, memory effect

High Performance DTC Design Example

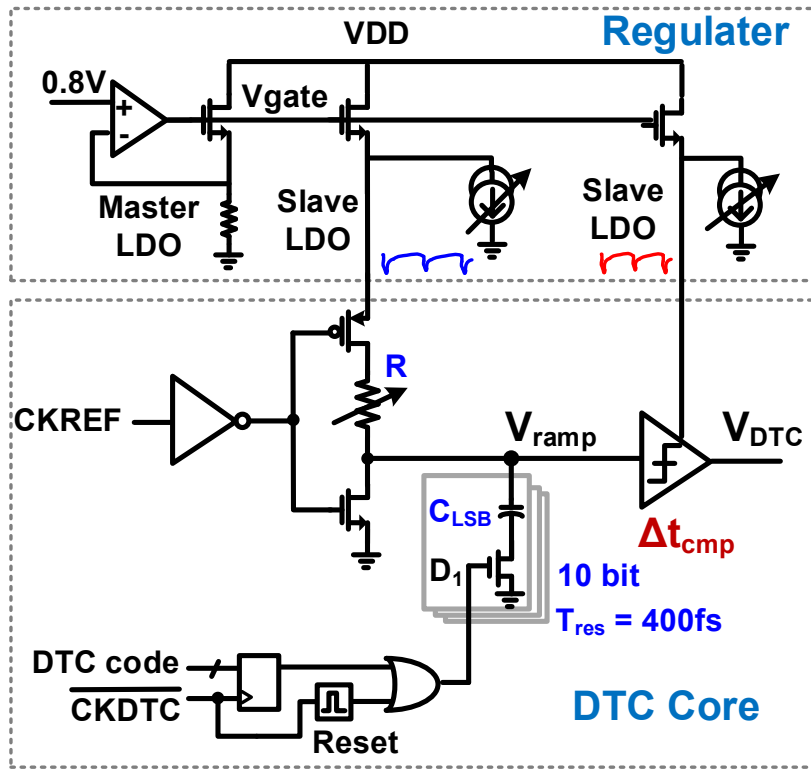


- DTC code reset to “1” each cycle to fully discharge tuning cap.

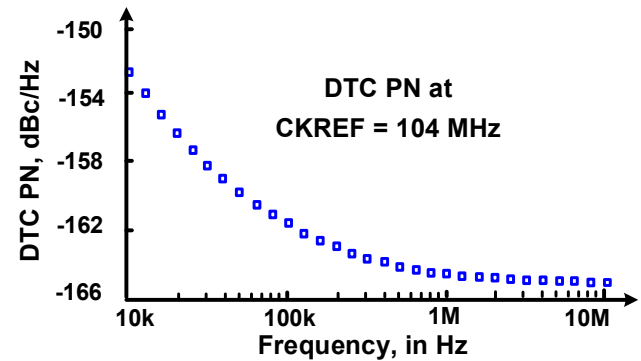  - Master-slave regulator for fast settling
- Bleeding current
↑ gm/C to speed up settling
at cost of higher I_{dc}
- Programmable R cover process variation




[W. Wu JSSC Dec 2021]

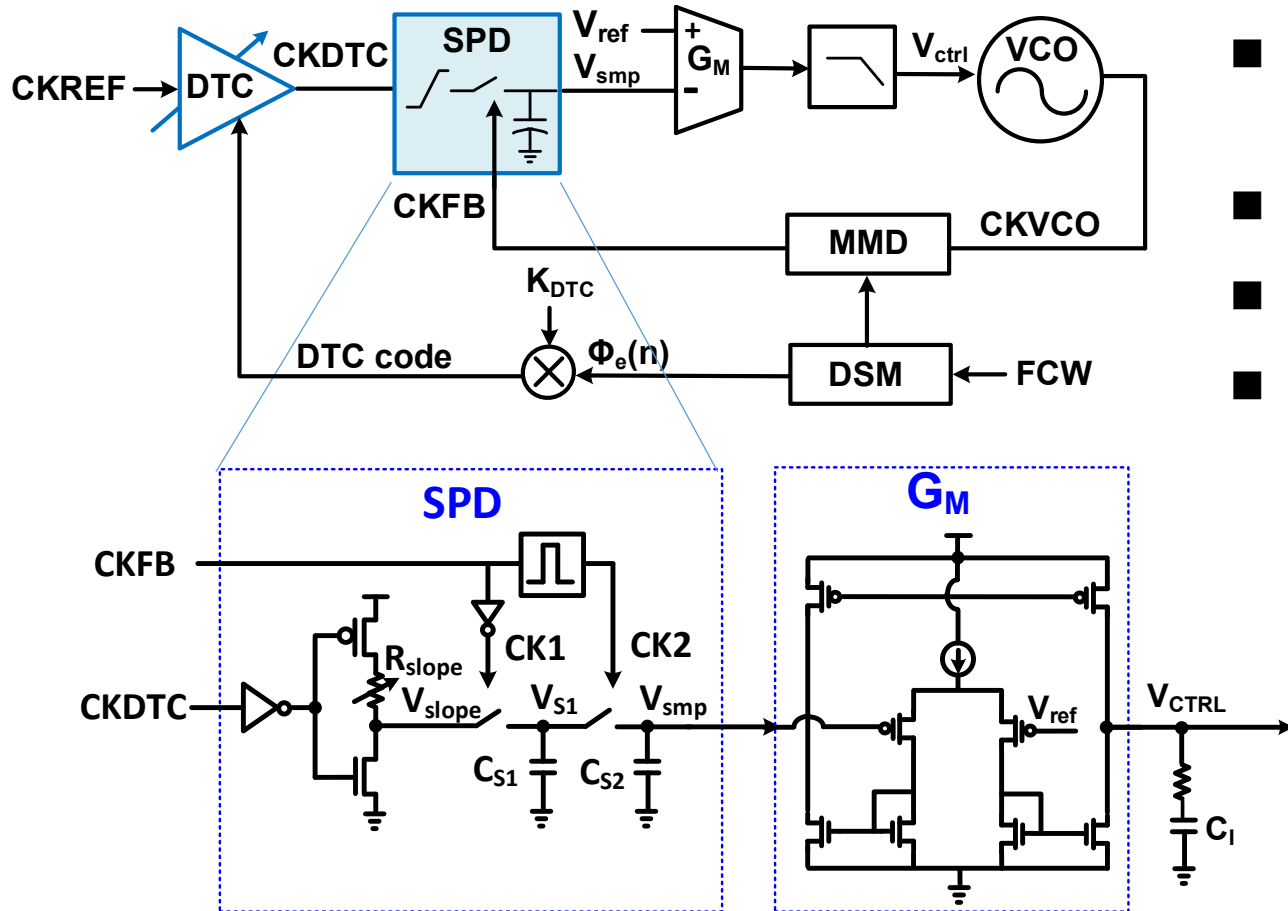
Continue with DTC-Assisted PD in Analog PLL



 
- V_{smp} is ZOH: 1st-order IIR filtering
- $K_{SPD} = K_{slope} / (2\pi f_{ref})$, for $K_{slope} = 6\text{GV/s}$, $f_{ref} = 104\text{ MHz}$, $\rightarrow K_{SPD} = 57/2\pi \gg K_{PD}$ in PFD-CP PLL
- G_M can be μA , its noise suppressed by high K_{SPD}
- Linearity of SPD not critical as DTC cancels QE
- Noise: $\sim 200\text{fF } C_{s1,2}$ results in $< -170\text{dBc/Hz}$




Constant Slope DTC (I/C)

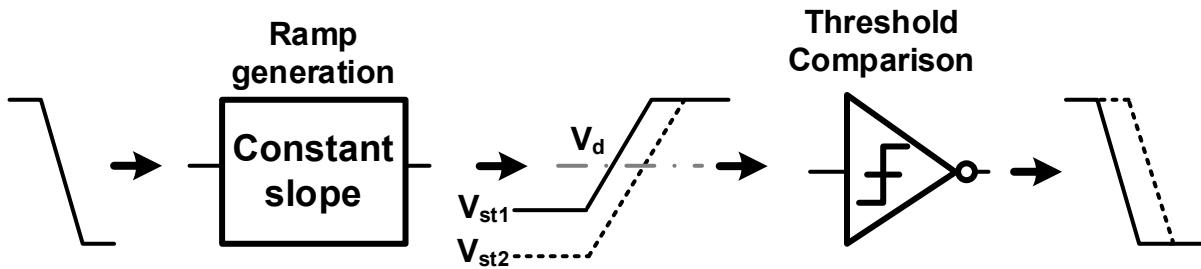

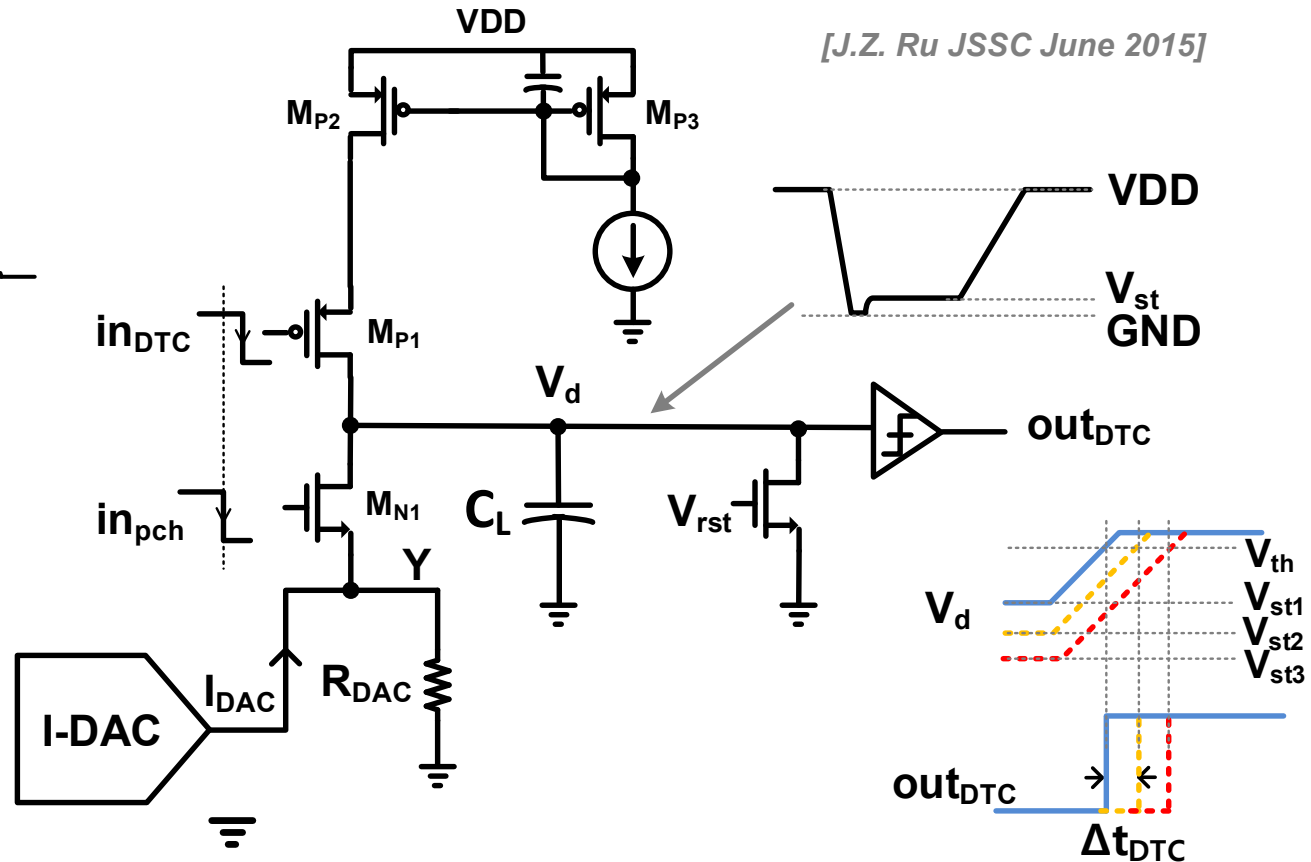- **Pros: no slope dependent delay**
- **Cons:**
 - **Nonlinearity sources:** I varies with code due to channel length mod., V_{st} settling error, etc.
 - **Flicker noise** from I
 - **Need high VDD** for high performance (e.g., 1.5V)



 
$$\Delta t_{DTC} = \int_{V_{st}}^{V_{th}} \frac{C_L(V)}{I_G(V)} dV$$




[J.Z. Ru JSSC June 2015]

Inverse-Constant-Slope DTC for Coarse-Fine DTC

Constant slope DTC

 

 
$$\Delta t_{DTC} = \int_{V_{st}}^{V_{th}} \frac{C_L(V)}{I_G(V)} dV$$




- DTC delay controlled by voltage V_{pch}
- Linearity affected to $I_G(V)$ and $C(V)$
- Linearity affected by DAC

ICS-DTC

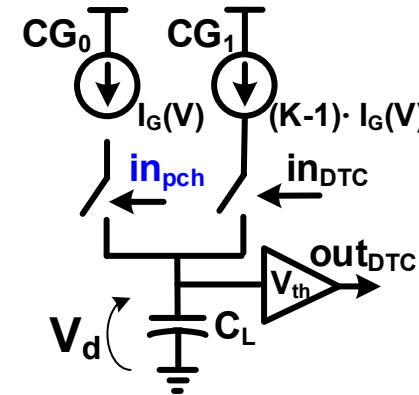
 
$$\Delta t_{DTC} = \int_0^{V_{th}} \frac{C_L(V)}{K \cdot I_G(V)} dV - \frac{\Delta t_{pch}}{K}$$




- controlled by time T_{pch}
- immunity to $I_G(V)$ and $C(V)$
- no need DAC





Too coarse, need another fine DTC

T_{pch} , T_{dTC} gen. uses DFFs and mux at f_{vco} 22

[S. M. Dartizio ISSCC 2023]

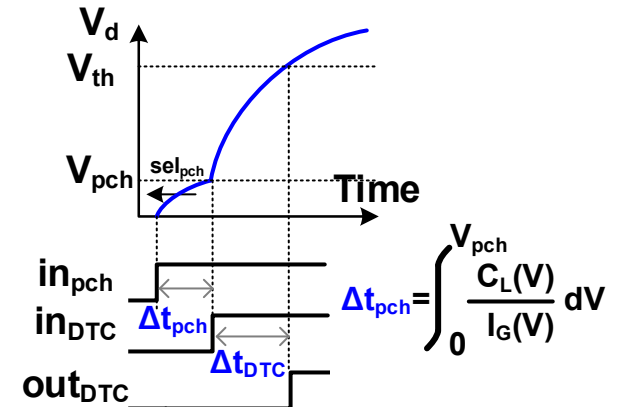

 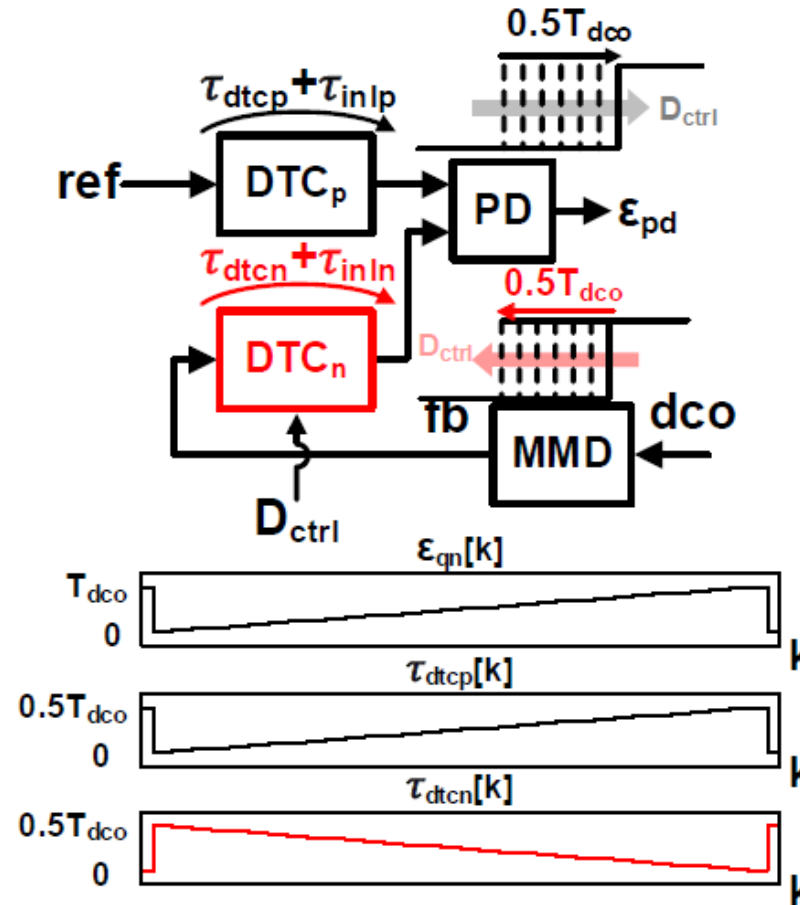 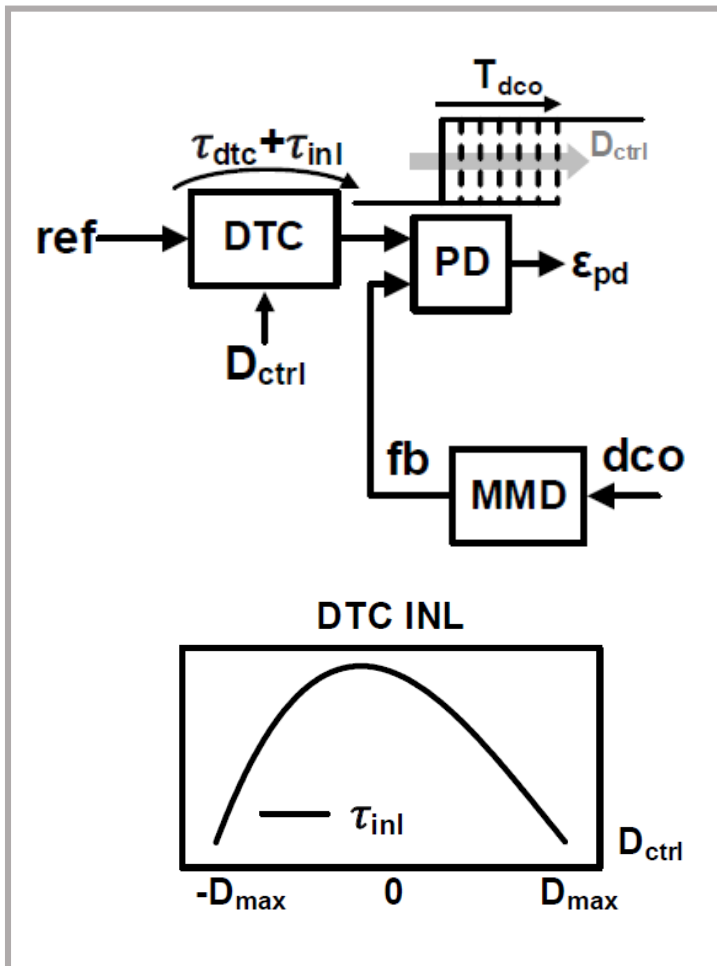Pseudo-Differential DTC for Better Linearity



$$\begin{aligned} \tau_{indiff}(D_{ctrl}) &= \tau_{inlp}(D_{ctrl}) - \tau_{inln}(D_{ctrl}) \\ &= 2b_1 \frac{D_{ctrl}}{2D_{max}} \left(1 - 4\left(\frac{D_{ctrl}}{2D_{max}}\right)^2\right) \end{aligned}$$

only odd-symmetric components

[D. Xu ISSCC 2024]

- Two half-range DTCs \rightarrow each DTC has better linearity
- Even-symmetric INL cancels

Digital Assisted Techniques for Linear DTC

- **DTC nonlinearity calibration (NLC)**
- **Reverse-Concavity Variable-Slope DTC**
- **DTC range reduction with multiple VCO/DCO phases**


Will be discussed next in digital calibration section

Outline

- Fractional-N PLL Design Challenges
- PLL Architecture Review
- DTC-Assisted Phase Detector Design
- **Digital Calibrations to Enhance PLL Performance**
 - **DTC Gain CAL, NLC, Range Reduction**
- LO Chain Design Example for 5G NR

Adaptive Filter Used in DPLL for Calibration


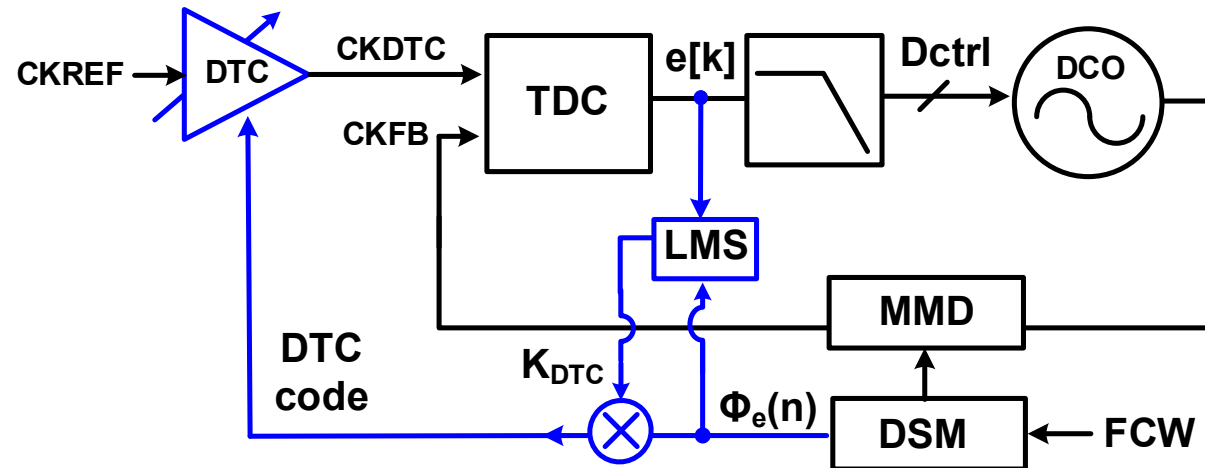
DTC gain need to be accurate to ensure QN cancellation




For DTC gain calibration:

- $h(k)$ is K_{DTC}
- Input signal $x(k)$: accumulated QE due to DSM, i.e., Φ_e .
- Error signal $e(k)$: phase error between CKREF and CKFB
- CKDTC phase is the output signal $y(k)$
- CKFB phase is the desired output signal $d(k)$


LMS adaptation

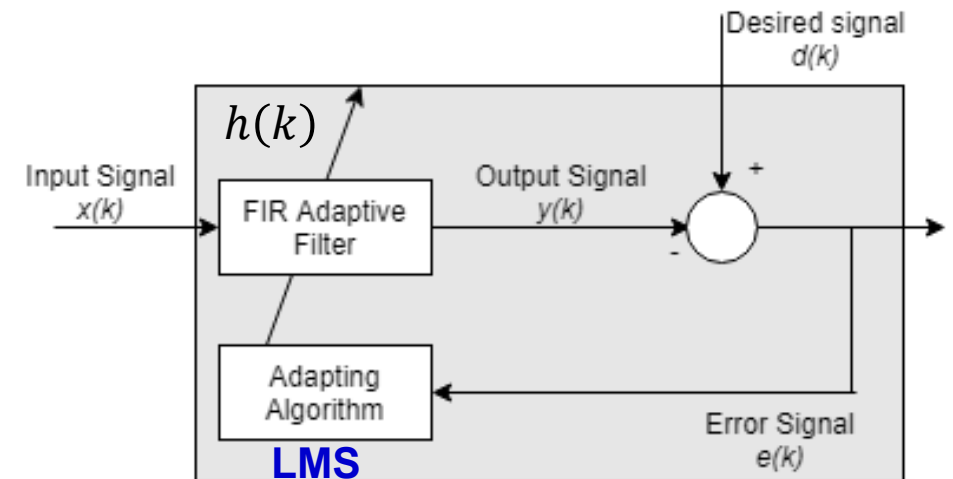 


DTC Gain CAL in Analog Sampling PLL [1]

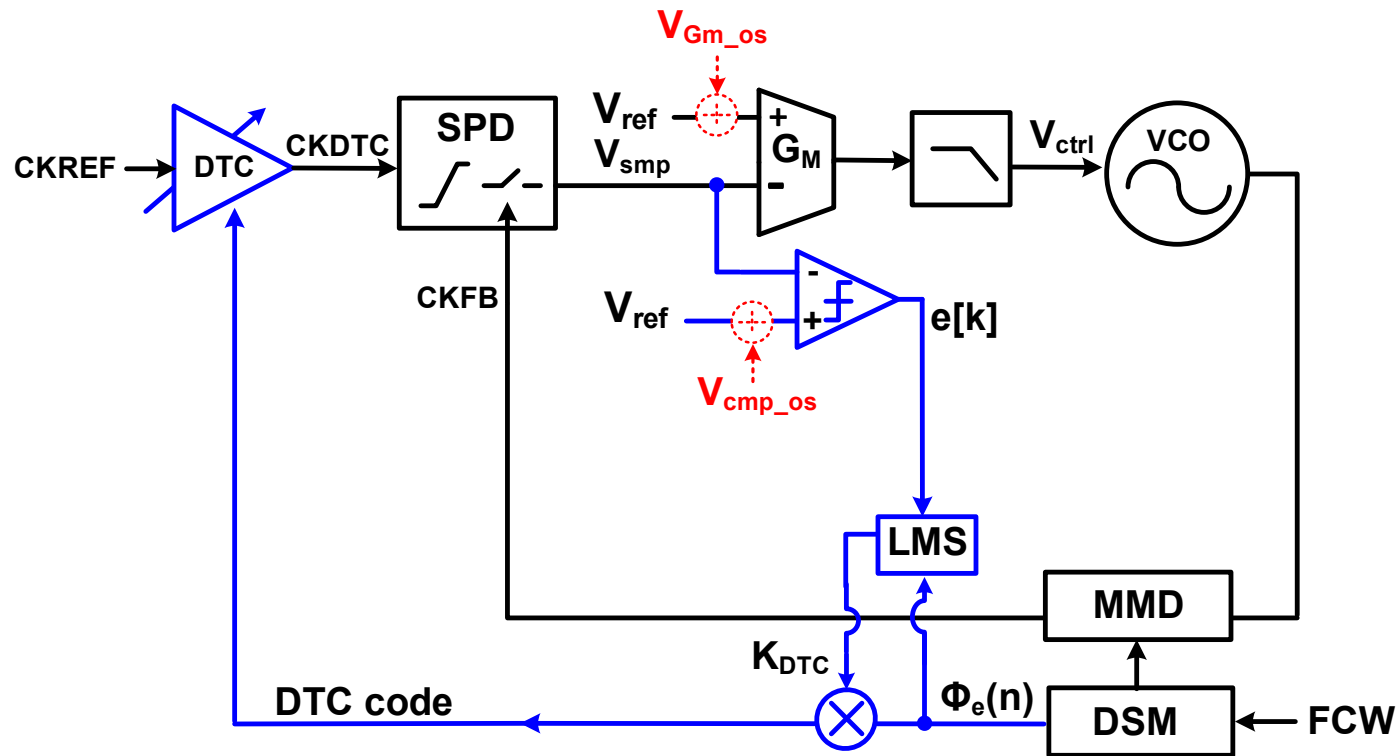


■ Issues of comparator, G_M offset

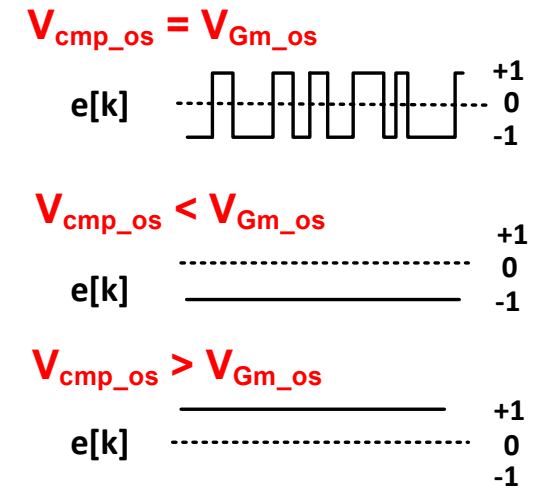

LMS adaptation

 


DTC Gain CAL in Analog Sampling PLL [2]

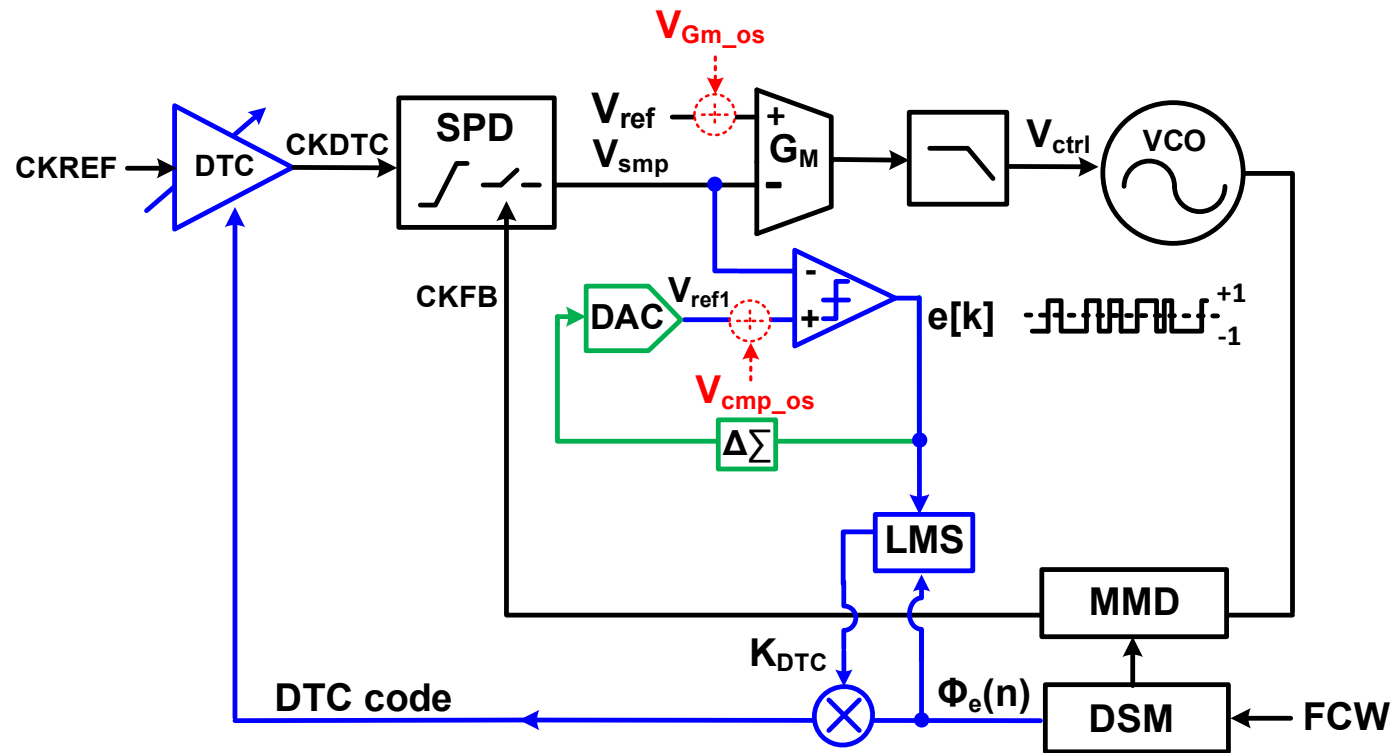

- Single comparator gets sign of PHE, $e[k] \rightarrow$ LMS
- Remove DC offset in $e[k]$ by adjusting V_{ref1}
- Simple 1-bit ΔV -DAC is sufficient


Alternative Way to Get Zero-Mean PHE Sign [1]

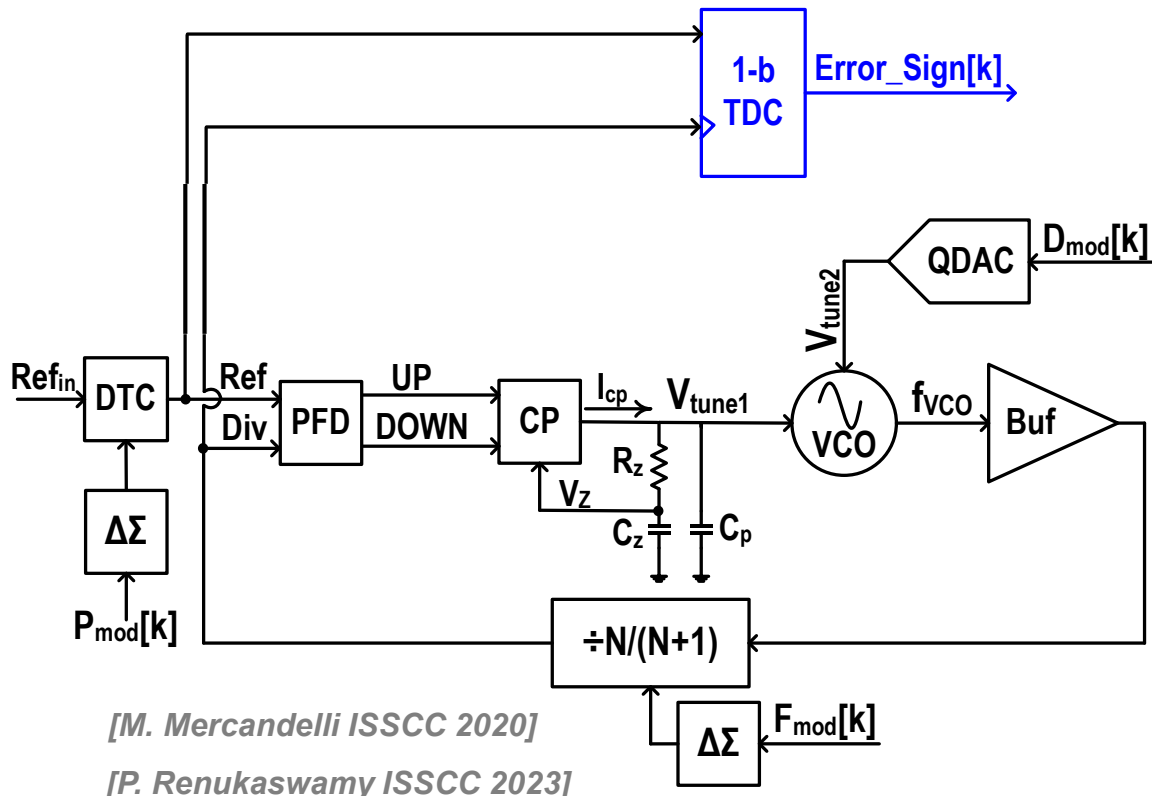- Phase offset (ΔT_{of}) varies over PVT
- Use coarse-fine DTC to compensate $\Delta T_{of} \rightarrow$ POC-DTC tracks ΔT_{of} over PVT
- Error_Sign[k] is zero-mean after convergence




[M. Mercandelli ISSCC 2020]


[P. Renukaswamy ISSCC 2023]

 

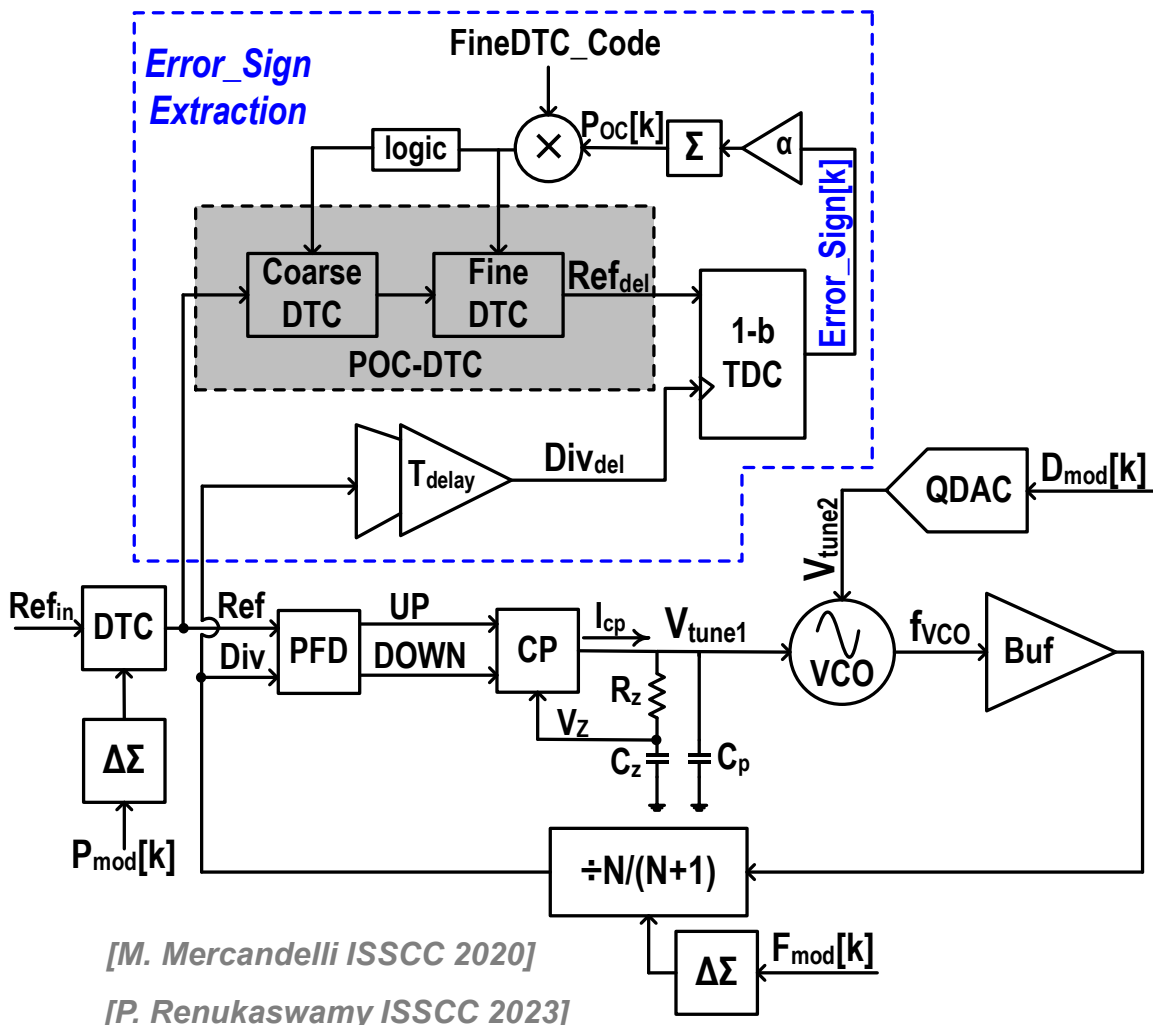Alternative Way to Get Zero-Mean PHE Sign [2]




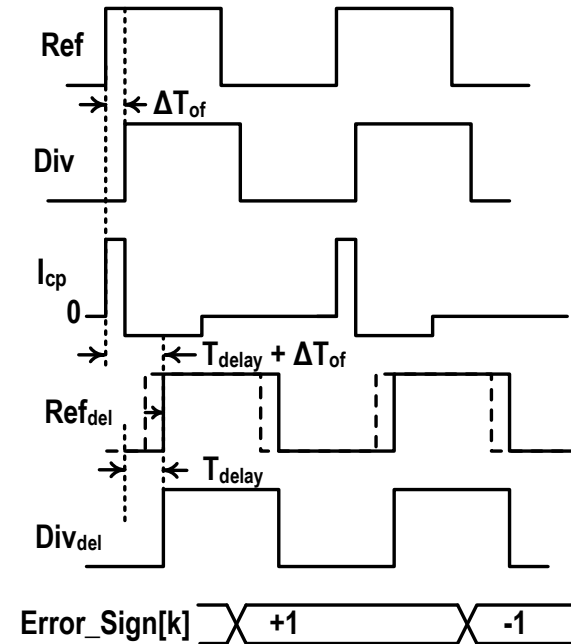- Phase offset (ΔT_{of}) varies over PVT
- Use coarse-fine DTC to compensate $\Delta T_{of} \rightarrow$ POC-DTC tracks ΔT_{off} over PVT
- Error_Sign[k] is zero-mean after convergence





DTC NLC – Polynomial CAL

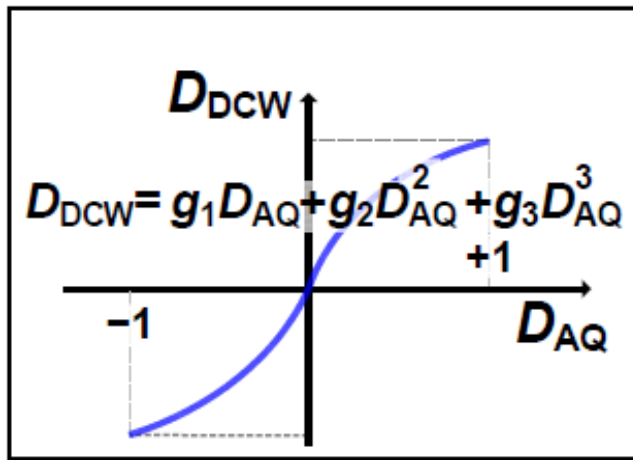- Intrinsic INL of a RC-delay based DTC has strong 2nd order NL
- Use LMS loop to get DTC gain (g_1), as well as its 2nd and 3rd order component (g_2 and g_3); D_{AQ} is accumulated DSM phase error, $\Phi_e(n)$




[H. Park ISSCC 2021]

 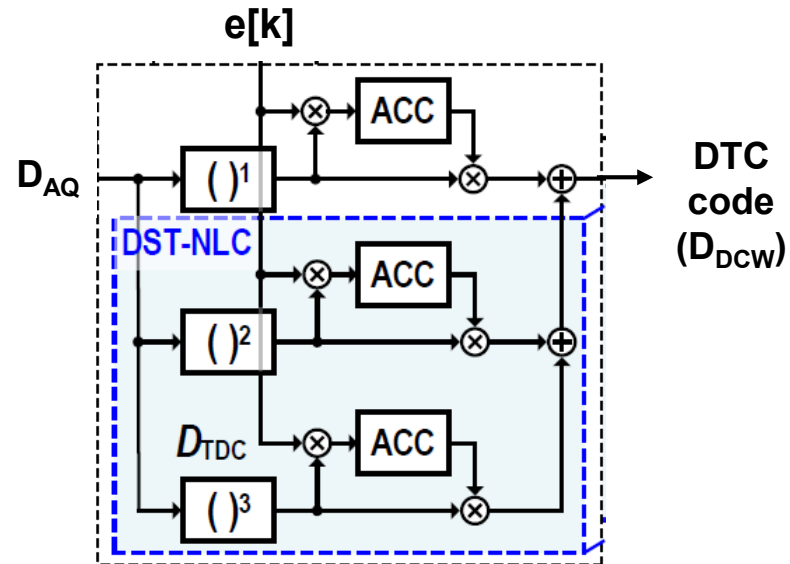


Reverse-Concavity Variable-Slope DTC

Conventional variable-slope DTC

 

 - Change R_U to compensate NL
- Voltage DAC controls R_U
- Adaptation loop find DAC code



[M.Rossoni ISSCC 2024]


DTC Range Reduction for Better Linearity

Recap DTC tradeoffs


- DTC Delay Range (DR): $DR \propto T_{VCO}$, DSM order
- DTC QN $\propto t_{res}^2$ $DR = 2^n \cdot t_{res} = 2^n \cdot \ln 2 \cdot RC_{LSB}$
- DTC thermal noise $\mathcal{L} \propto DR$: $\mathcal{L} \cong 10 \cdot \log_{10} \left[2kT \cdot f_{ref} \frac{(2\pi)^2}{\ln 2} \cdot DR \cdot R \right]$
- DTC linearity better for smaller DR
- DTC power $\propto DR^2$

$DR \downarrow \rightarrow$ less bits, faster slope, lower noise and power, more linear


Half DTC Range with Two VCO Phases

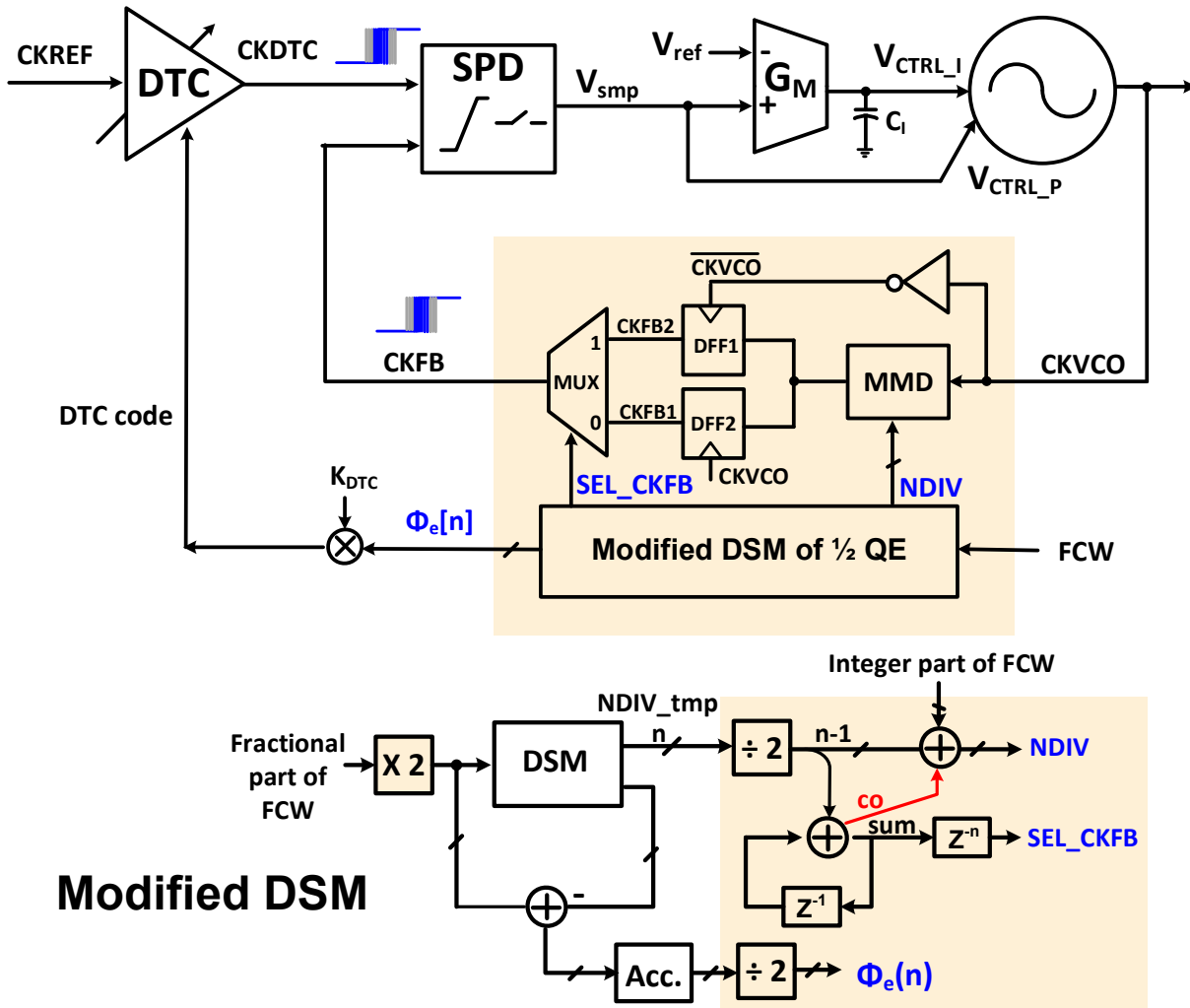

Example of a MASH1 DSM

 

Example of a MASH1-1 DSM

 



— Proposed MMD and DSM

— Conventional MMD and DSM


■ Switching from CKFB1 to CKFB2 introduces a half-period delay

[W. Wu ISSCC 2021]

 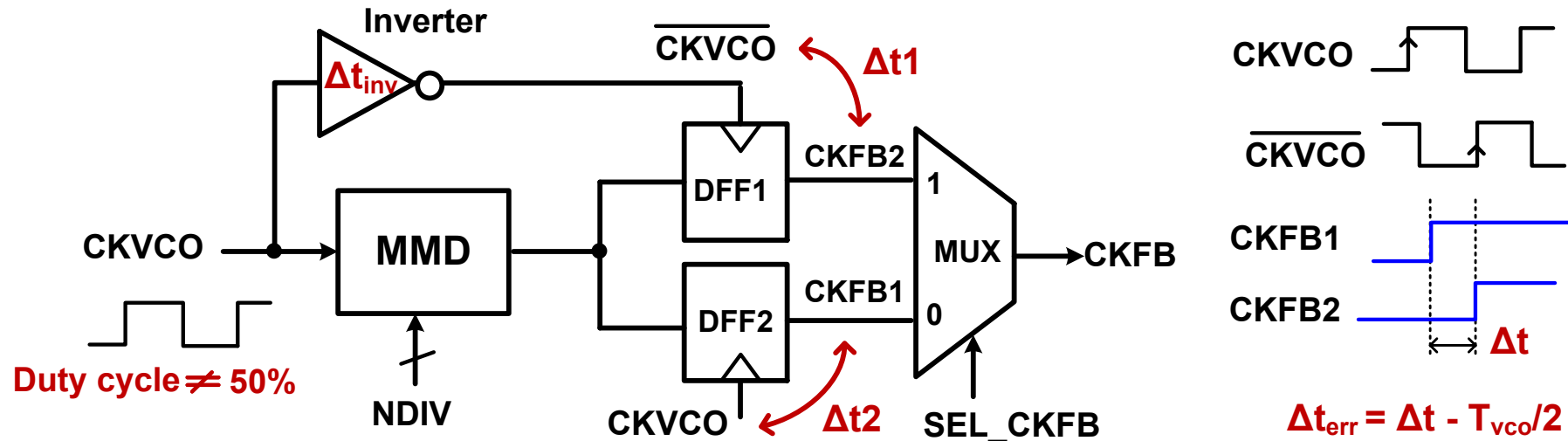VCO Duty Cycle Error Disrupts K_{DTC} CAL




VCO Duty Cycle Calibration

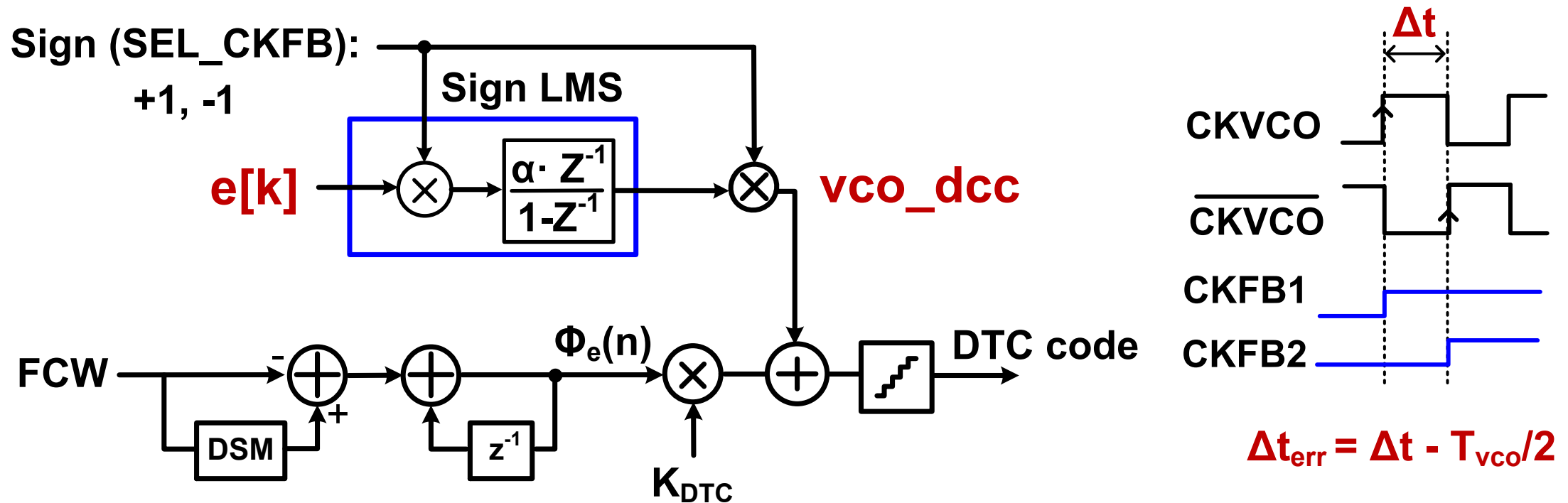

- SEL_CKFB = +1 \rightarrow push back CKDTC by $\Delta t_{err}/2$
- SEL_CKFB = -1 \rightarrow pull-in CKDTC by $\Delta t_{err}/2$




Simulated K_{DTC} CAL and DTC Code

 


- **KDTC converges < 30 μs , even with 12% VCO duty cycle error**
- **DTC code range is halved**

1/8 DTC Range Reduction Using 8 RO Phases

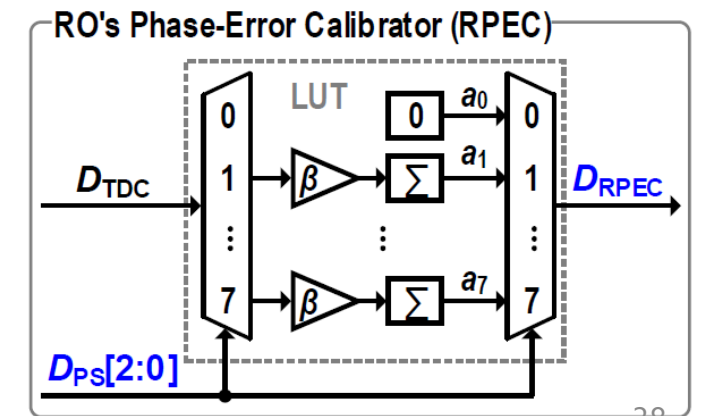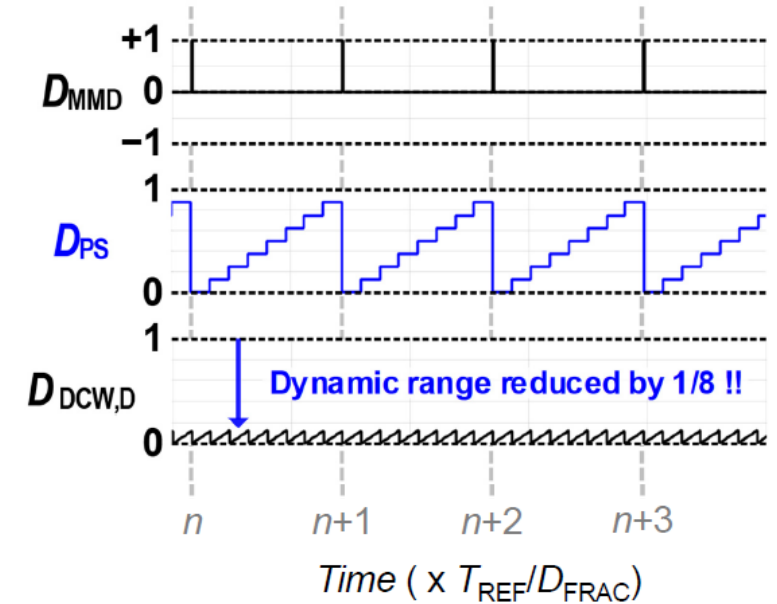
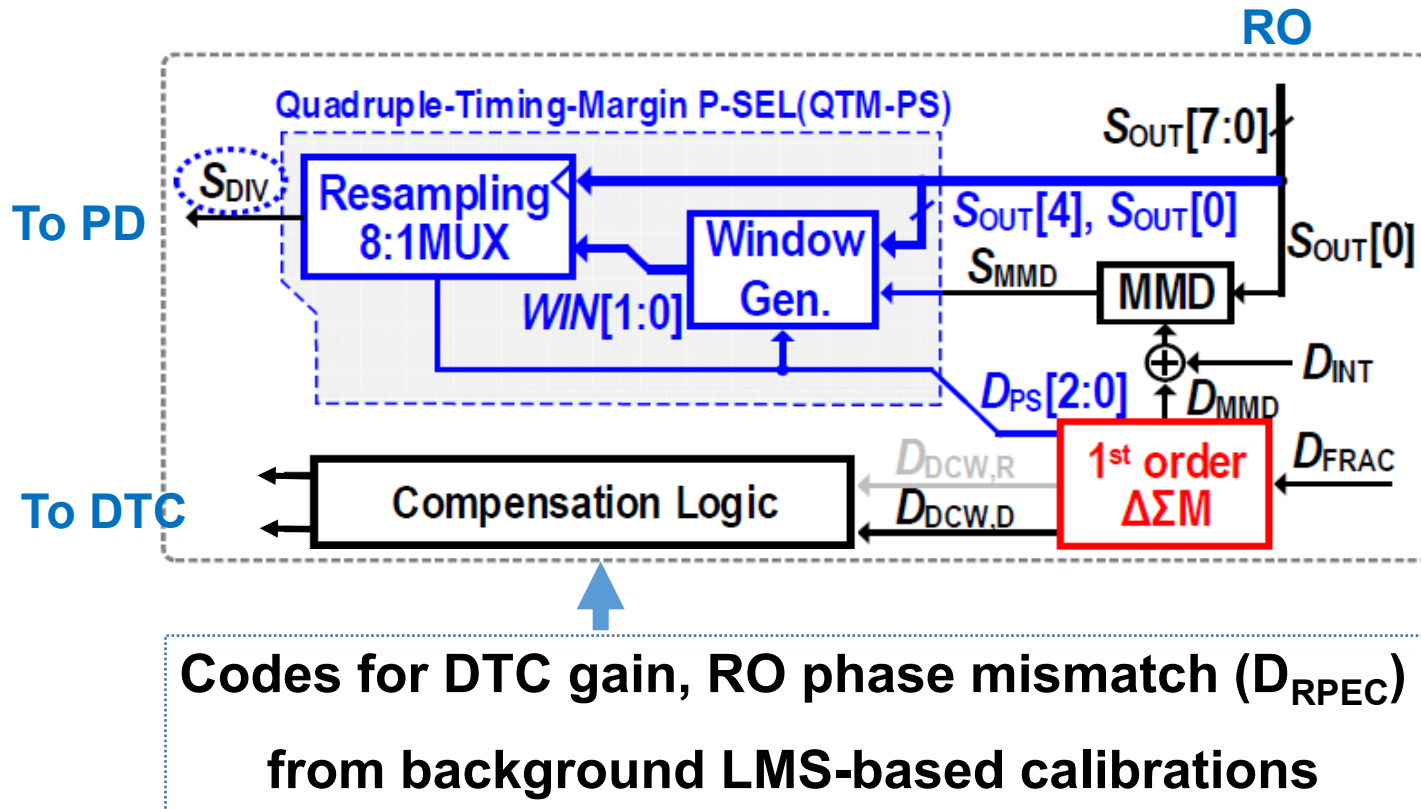
- $S_{OUT}[7:0]$ are 8 phases from differential ring oscillator
- Timing of QTM-PS is stringent



Low Jitter Sampling Analog PLL Example


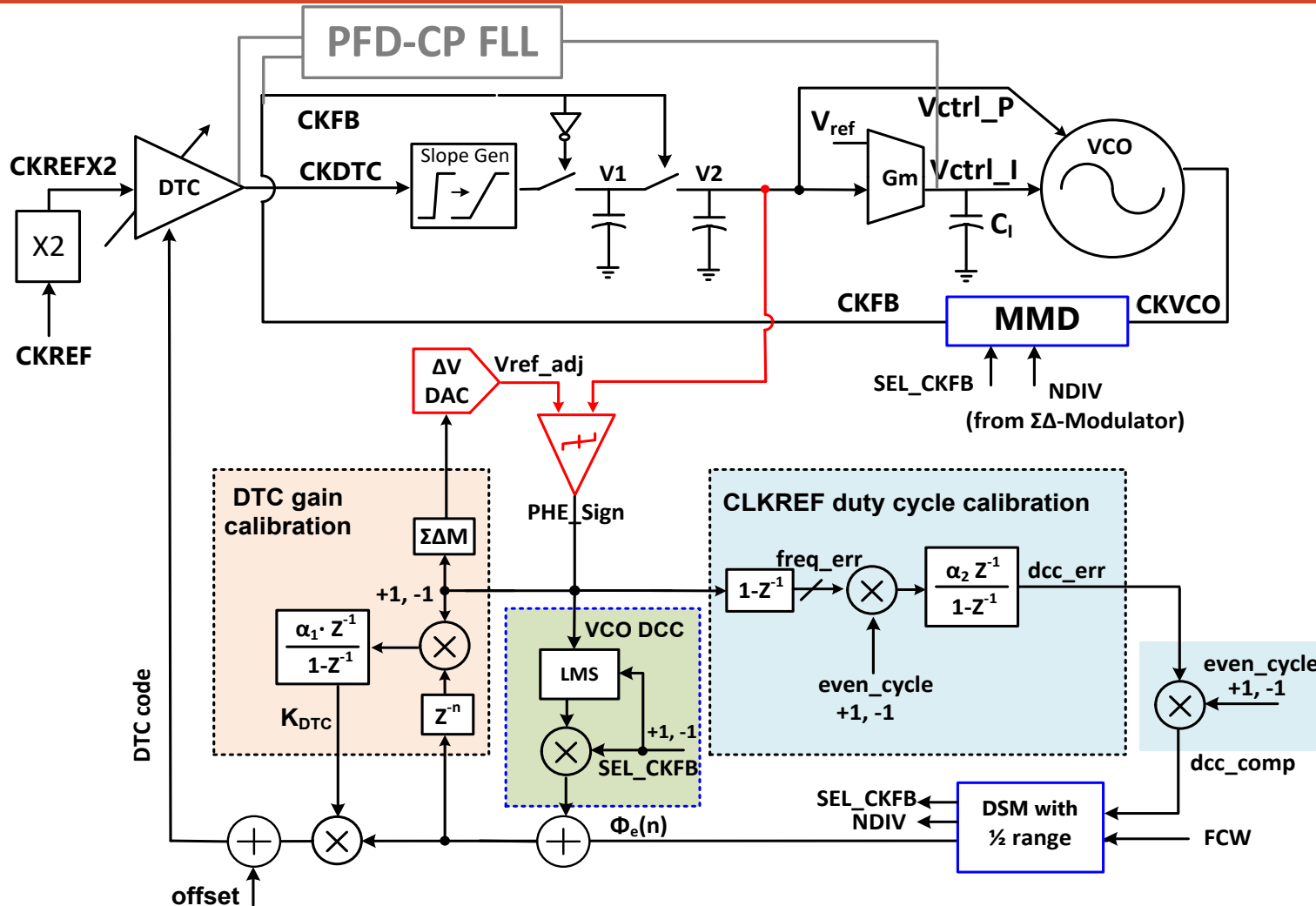


■ 14nm FINFET, Core 0.31mm²

  


[W. Wu ISSCC 2021]

Simulated Background Calibration

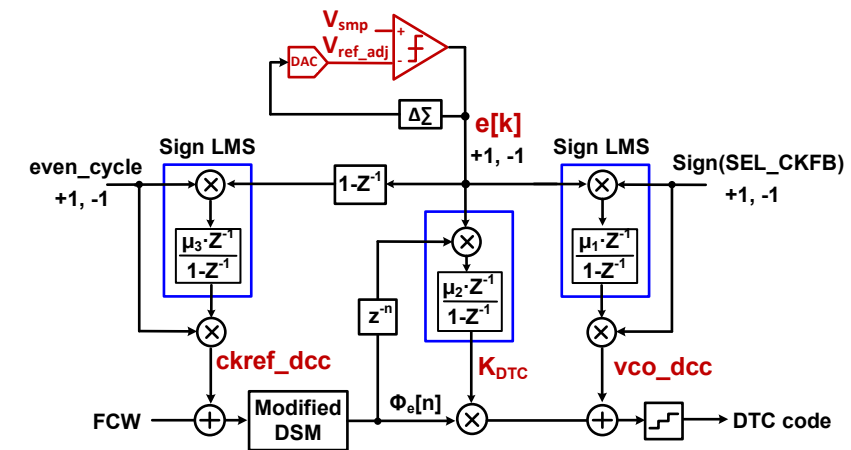 


- All calibrations converge $< 30\mu s$ and track PVT
- Works robustly for both integer and fractional channels


Measured Fractional-N Spurs and Jitter

 

[W. Wu ISSCC 2021]

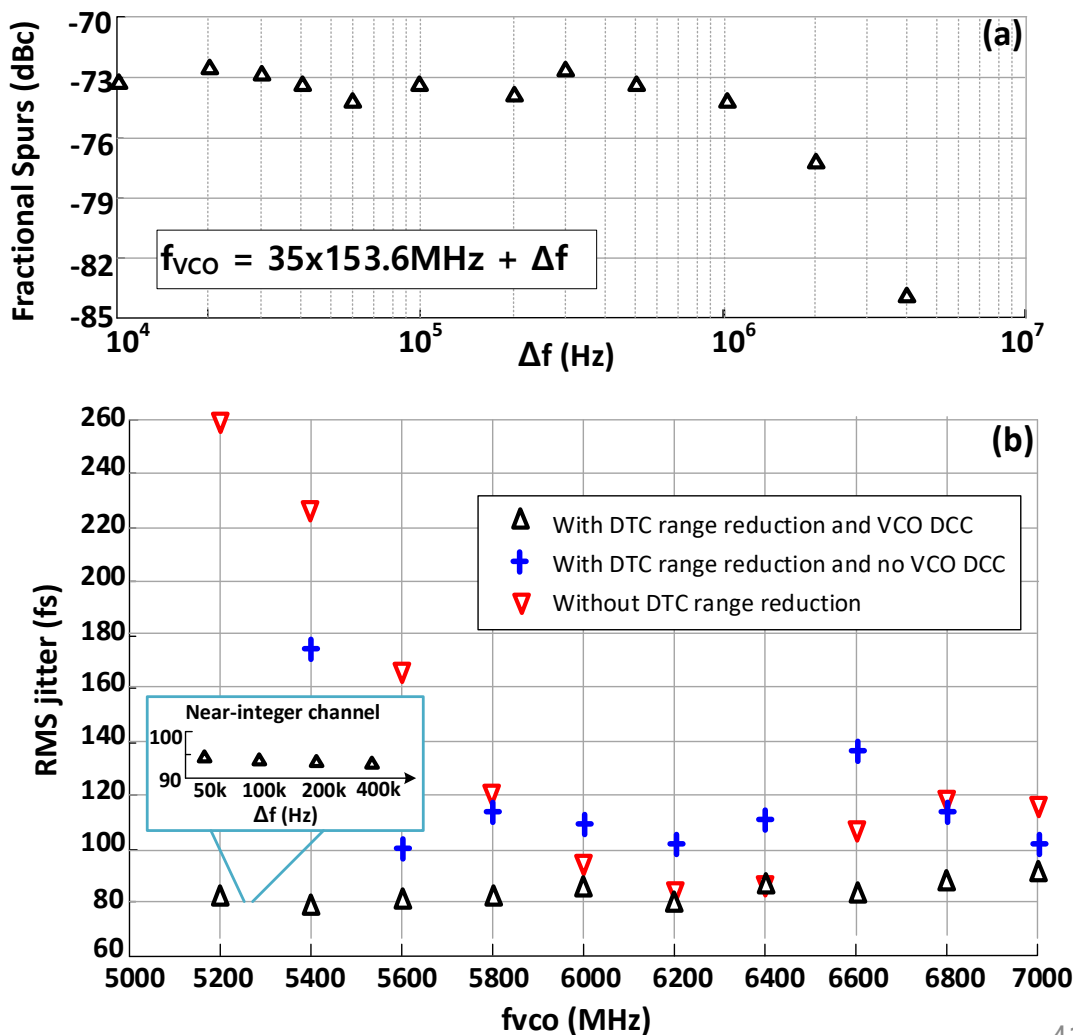

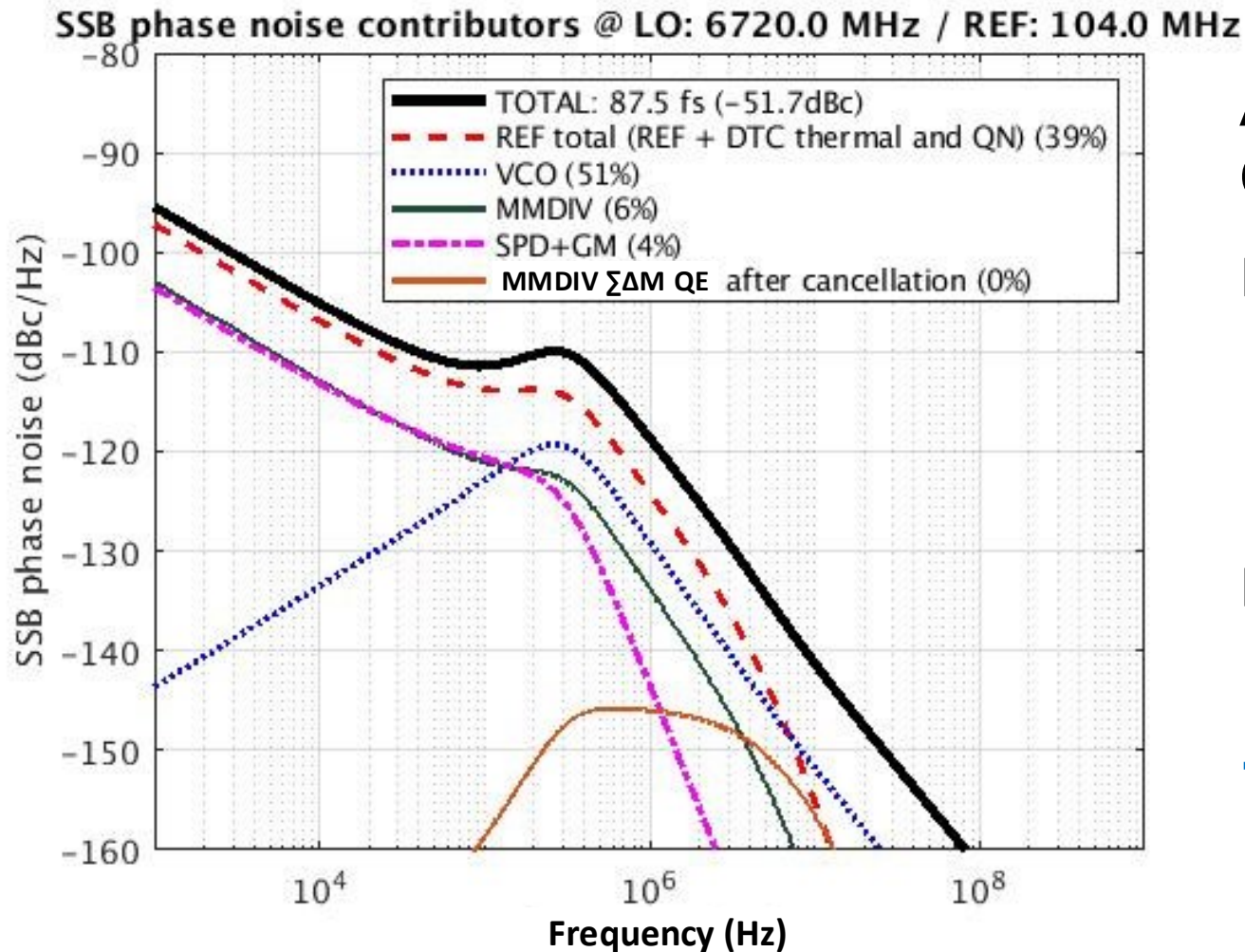PN Contributors in Low-Jitter DTC-Assisted PLL




After suppress noise from PD, DSM QN, MMD →

- PLL IPN is dominated by
 - CKREF – external clock ref.
 - VCO/DCO
 - PLL BW is chosen to tradeoff the contribution of the two
- Common for any PLLs

Outline

- Fractional-N PLL Design Challenges
- PLL Architecture Review
- DTC-Assisted Phase Detector Design
- Digital Calibrations to Enhance PLL Performance
- **LO Chain Design Example for 5G NR**

5G New Radio Frequency Bands

 


5G FR2 Band	Uplink/Downlink (GHz)	Channel bandwidth (MHz)
N257	TDD 26.5 – 29.5	50, 100, 200, 400
N258	TDD 24.25 – 27.5	50, 100, 200, 400
N259	TDD 39.5 – 43.5	50, 100, 200, 400
N260	TDD 37.0 – 40.0	50, 100, 200, 400
N261	TDD 27.5 – 28.35	50, 100, 200, 400

Smart Phones with 5G mmW Chipset

■ FR2 system


Modem + mmW IFIC + mmW AiP

 

<https://www.ifixit.com/Guide/Google+Pixel+7+Pro+5G+mmWave+Antenna+Replacement/154719>



 
<https://www.techinsights.com/blog/muratasamsung-2nd-gen-mmwave-aip-discovered-samsung-galaxy-a53>



<https://unitedlex.com/insights/apple-iphone-13-pro-max-teardown-report/>


LO Design Challenges for 5G mmW

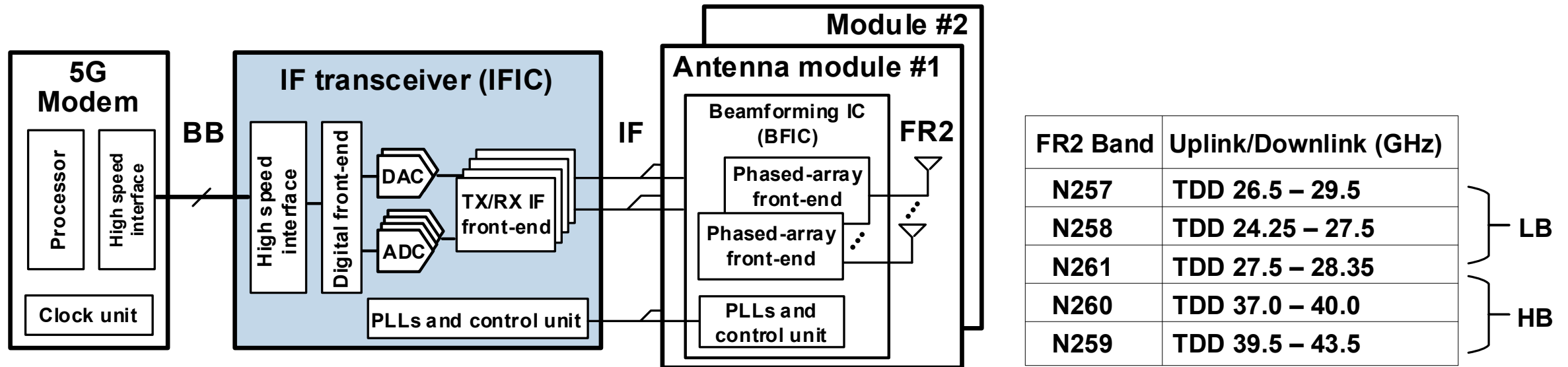

- mmW LO circuitry on **both IFIC and BFIC**
- Transceiver SNR is **limited by LO IPN**
- **Multi-band** support with **low power and low cost**
- **256-QAM** support demands **low jitter LO**



LO Topology Considerations

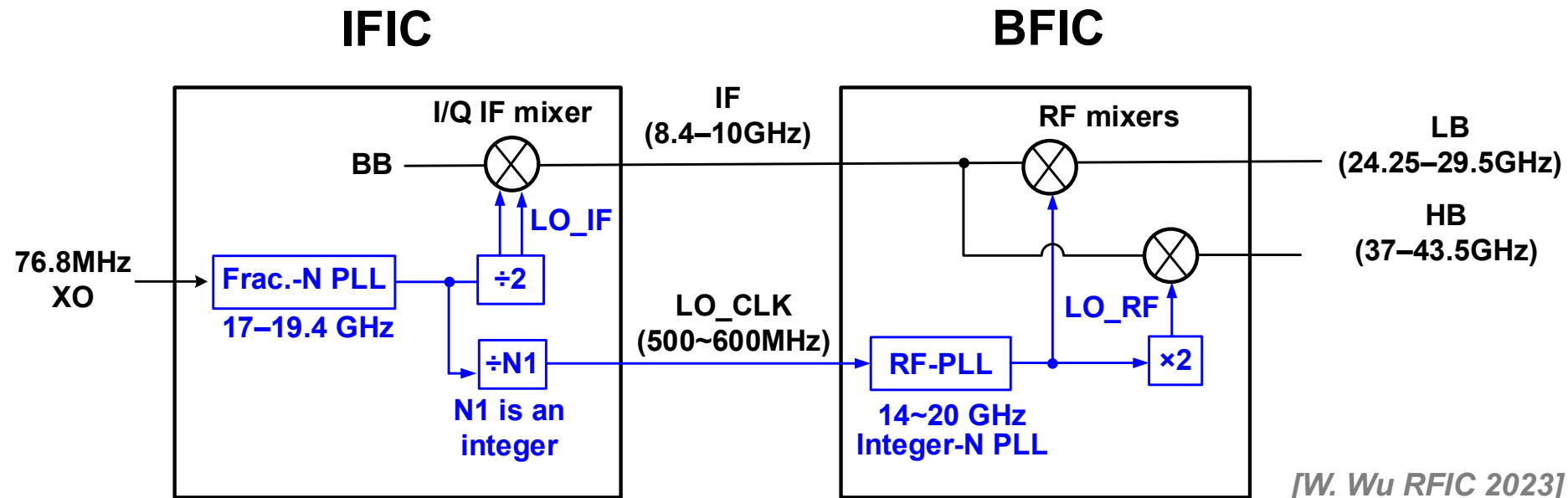- IFIC generates LO_IF & reference clock (LO_CLK) for BFIC
- Low-jitter frac.-N PLL dominates LO chain IPN
- BFIC PLL simplifies to an integer-N of wide BW (e.g., SSPLL)
 - Low-power as VCO PN is relaxed
 - Compact area: one wideband VCO for both LB and HB




Low-Jitter Fractional-N PLL Directly at mmW

 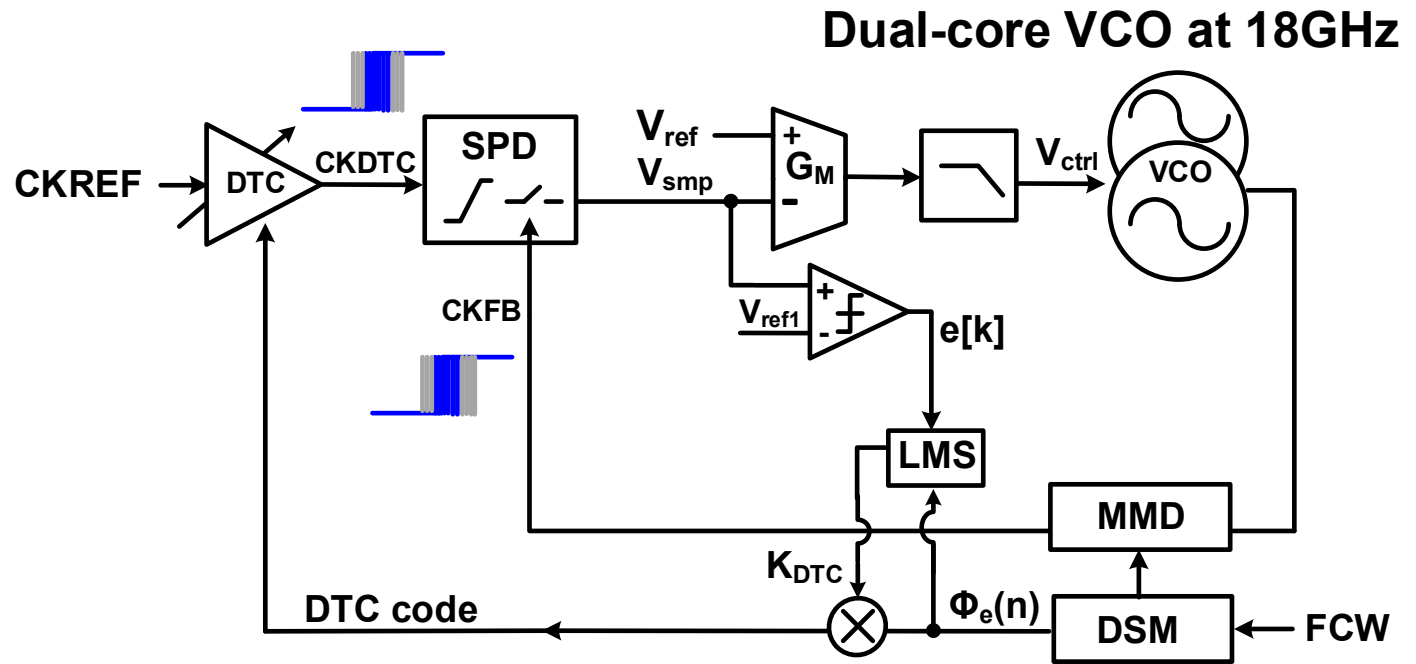- DTC-based sampling PLL
→ low jitter
- VCO operates at 18 GHz
→ no multiplier, low power
- Dual-core VCO → low jitter



[W. Wu RFIC 2023]

Low PN LC Oscillator Design

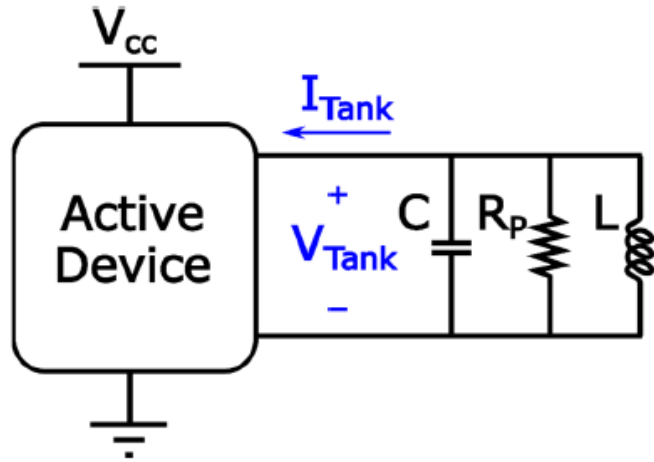


$$PN_{dB} = 10 \log_{10} \left[\left(\frac{\omega_0}{2Q\Delta\omega} \right)^2 \frac{2FkT}{P} \right] = 10 \log_{10} \left[\left(\frac{\omega_0}{\Delta\omega} \right)^2 \frac{FkT\omega_0}{V_{Tank}^2} \frac{L}{Q} \right]$$

$$\text{Resonator power } P = \frac{V_{Tank}^2}{2R_p} = \frac{V_{Tank}^2}{2\omega_0 L Q}$$

- V_{Tank} , F set by process
- Scaling L as long as $\frac{L}{Q}$ can be reduced to lower PN
- Beyond this limit \rightarrow use multi-core oscillator



$$L_{eq} = L/N, C_{eq} = N \cdot C \rightarrow \text{same } \omega_0, \text{ same } Q$$
 
$$PN_{multi-core} = PN_0 - 10 \log_{10}(N)$$



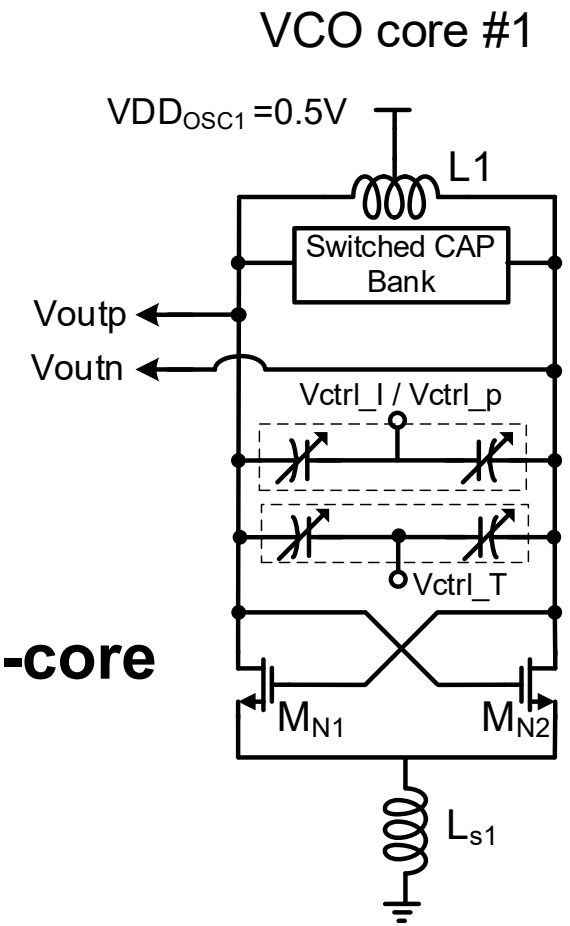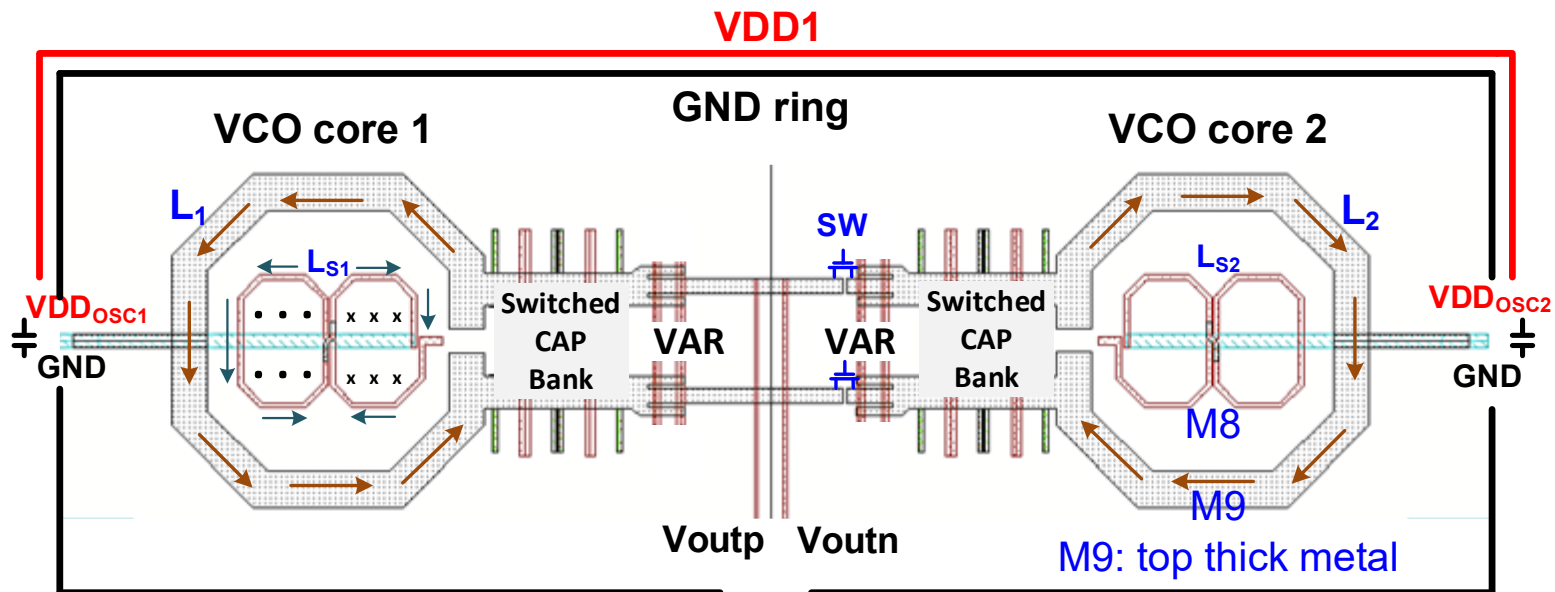[D. Murphy JSSC Nov 2018]

Switchable Dual-core VCO for Power, PN Tradeoff




- Good EM isolation, symmetrical → same f_{vco} for 1- or 2-core
- Figure-8 tail L_s put inside main L to save area
- N=1: -120 dBc/Hz @1MHz measured at 6GHz
- N=2: -122.5 dBc/Hz

[W. Wu ISSCC 2021]


LO Configuration to Further Improve IPN

- 256-QAM requires rms jitter of ~ 100 fs
- Hard to further reduce rms jitter of IF-PLL \rightarrow use two IF-PLLs
- PN of LO_IF and LO_RF are mostly uncorrelated \rightarrow lower chain IPN



Low-power mode for 64-QAM/QPSK

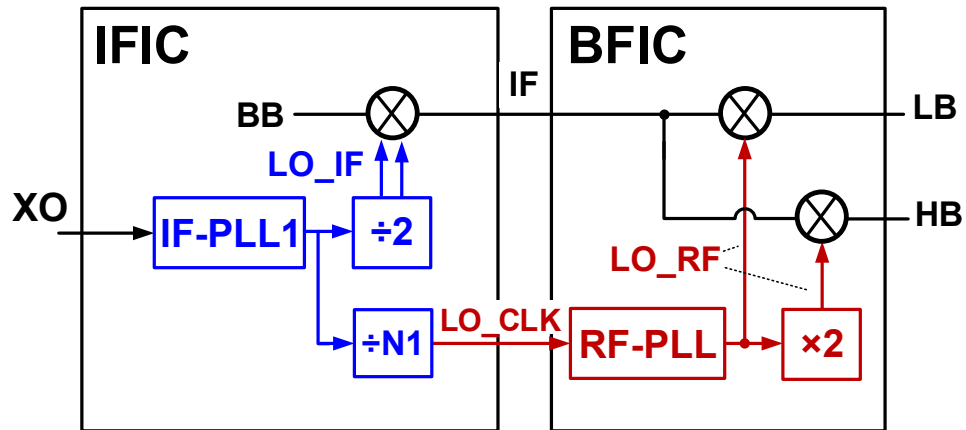

Low-jitter mode for 256-QAM

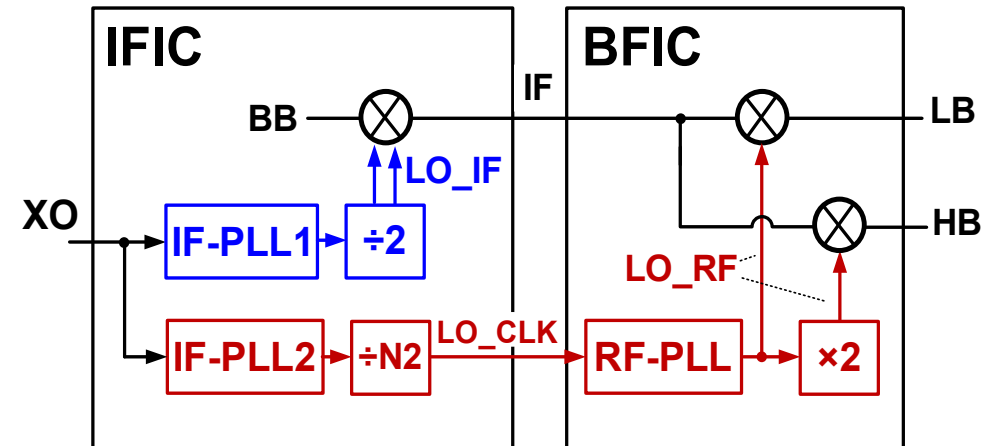

Measured Chain IPN at 28 GHz and 38 GHz

  

[W. Wu RFIC 2023, Samsung]

- Dual-PLL results in ~ 1.6 dB lower chain IPN
- -37.49 dBc IPN at 28 GHz \rightarrow EVM floor of 1.34%
- -34.29 dBc IPN at 38 GHz \rightarrow 112 fs rms jitter, EVM floor of 1.9%

Summary

- Advanced wireless application requires **frac. N PLLs of $< 100 f_{s_{rms}}$**
- PLLs with **DTC-assisted PD** have demonstrates low jitter, high FoM
- **DTC cancels DSM QE** → eases PD design
- Various design techniques aim to **improve DTC linearity**
- **Intensive digital calibrations** enhance PLL performance
- **Multi-core VCO** breaks design limit of single core with same VCO FoM

References [1]

- [1] X. Gao, E. A. M. Klumperink, P. F. J. Geraedts and B. Nauta, "Jitter analysis and a benchmarking figure-of-merit for phase-locked loops", in *IEEE Trans. Circuits Syst. II*, vol. 56, pp. 117-121, Feb. 2009.
- [2] D. Tasca et al., "A 2.9-to-4.0 GHz fractional- N digital PLL with bang-bang phase detector and 560 fsrms integrated jitter at 4.5 mW power," in *IEEE J. Solid-State Circuits*, vol. 46, no. 12, pp. 2745–2758, Dec. 2011.
- [3] N. Markulic et al., "A 10-bit, 550-fs step Digital-to-Time Converter in 28nm CMOS," in *Proc. 40th European Solid-State Circuits Conf. (ESSCIRC)*, Venice Lido, 2014, pp. 79–82.
- [4] J. Z. Ru et al., "A High-Linearity Digital-to-Time Converter Technique: Constant-Slope Charging," in *IEEE J. of Solid-State Circuits*, vol. 50, no. 6, pp. 1412-1423, June 2015.
- [5] S. Levantino et al., "An adaptive pre-distortion technique to mitigate the DTC nonlinearity in digital PLLs," in *IEEE J. Solid-State Circuits*, vol. 49, no.8, pp. 1762–1772, Aug. 2014.
- [6] C. Yao et al., "A 14-nm 0.14-ps_{rms} Fractional- N Digital PLL With a 0.2-ps Resolution ADC-Assisted Coarse/Fine-Conversion Chopping TDC and TDC Nonlinearity Calibration," in *IEEE J. Solid-State Circuits*, vol. 52, no. 12, pp. 3446–3457, Dec. 2017.
- [7] D. Murphy et al., "A 27-GHz Quad-Core CMOS Oscillator With No Mode Ambiguity", in *IEEE J. Solid-State Circuits*, vol. 53, no. 11, pp. 3208-3216, Nov. 2018.
- [8] S. A. Ahmadi-Mehr et al., "Analysis and Design of a Multi-Core Oscillator for Ultra-Low Phase Noise," in *IEEE Transactions on Circuits and Systems I: Regular Papers*, vol. 63, no. 4, pp. 529-539, April 2016.
- [9] D. Griffith et al., "An Integrated BAW Oscillator with $\leq \pm 30$ ppm Frequency Stability Over Temperature, Package Stress, and Aging Suitable for High-Volume Production," in *IEEE Int. Solid-State Circuits Conf. (ISSCC) Dig. Tech. Papers*, San Francisco, CA, pp. 58-60, Feb. 2020.
- [10] B. Bahr, A. Kiaei, M. Chowdhury, B. Cook, S. Sankaran and B. Haroun, "Near-Field-Coupled Bondless BAW Oscillators in WCSP Package with 46fs Jitter," *2021 IEEE Radio Frequency Integrated Circuits Symposium (RFIC)*, 2021, pp. 155-158.
- [11] D. Yang et al., "A Sub-100MHz Reference-Driven 25-to-28GHz Fractional- N PLL with -250 dB FoM," *2022 IEEE International Solid-State Circuits Conference (ISSCC)*, San Francisco, CA, USA, 2022, pp. 384-386
- [12] S. Kalia et al., "A Sub-100fs JitterRMS, 20-GHz Fractional- N Analog PLL using a BAW Resonator Based 2.5GHz On-Chip Reference in 22-nm FD-SOI Process," *2021 IEEE Radio Frequency Integrated Circuits Symposium (RFIC)*, 2021, pp. 151-154.
- [13] . Jung et al., "A 52MHz -158.2dBc/Hz PN @ 100kHz Digitally Controlled Crystal Oscillator Utilizing a Capacitive-Load-Dependent Dynamic Feedback Resistor in 28nm CMOS," *2022 IEEE International Solid- State Circuits Conference (ISSCC)*, 2022, pp. 60-62.

References [2]

- [14] C. Hwang, H. Park, T. Seong and J. Choi, "A 188fsrms-Jitter and -243dBc -FoM jitter 5.2GHz-Ring-DCO-Based Fractional-N Digital PLL with a 1/8 DTC-Range-Reduction Technique Using a Quadruple-Timing-Margin Phase Selector," *2022 IEEE International Solid-State Circuits Conference (ISSCC)*, 2022, pp. 378-380.
- [15] A. Franceschin, D. Riccardi and A. Mazzanti, "Series-Resonance BiCMOS VCO with Phase Noise of -138dBc/Hz at 1MHz Offset from 10GHz and -190dBc/Hz FoM," *2022 IEEE International Solid-State Circuits Conference (ISSCC)*, 2022, pp. 1-3.
- [16] H. Park, C. Hwang, T. Seong, Y. Lee and J. Choi, "32.1 A 365fsrms-Jitter and -63dBc -Fractional Spur 5.3GHz-Ring-DCO-Based Fractional-N DPLL Using a DTC Second/Third-Order Nonlinearity Cancellation and a Probability-Density-Shaping $\Delta\Sigma$," *2021 IEEE International Solid-State Circuits Conference (ISSCC)*, 2021, pp. 442-444.
- [17] W. Wu et al., "A 14-nm Ultra-Low Jitter Fractional-N PLL Using a DTC Range Reduction Technique and a Reconfigurable Dual-Core VCO," in *IEEE Journal of Solid-State Circuits*, vol. 56, no. 12, pp. 3756-3767, Dec. 2021.
- [18] E. Thaller et al., "A K-Band 12.1-to-16.6GHz Subsampling ADPLL with 47.3fsrms Jitter Based on a Stochastic Flash TDC and Coupled Dual-Core DCO in 16nm FinFET CMOS," in *IEEE Int. Solid-State Circuits Conf. (ISSCC) Dig. Tech. Papers*, San Francisco, CA, pp. 451-453, Feb. 2021.
- [19] D. Turker et al., "A 7.4-to-14GHz PLL with 54fsrms jitter in 16nm FinFET for integrated RF-data-converter SoCs," in *IEEE Int. Solid-State Circuits Conf. (ISSCC) Dig. Tech. Papers*, San Francisco, CA, pp. 378-380, Feb. 2018.
- [20] Y. Hu et al., "A 21.7-to-26.5GHz Charge-Sharing Locking Quadrature PLL with Implicit Digital Frequency-Tracking Loop Achieving 75fs Jitter and -250dB FoM," in *IEEE Int. Solid-State Circuits Conf. (ISSCC) Dig. Tech. Papers*, San Francisco, CA, pp. 276-278, Feb. 2020.
- [21] J. Kim et al., "A 76 fsrms Jitter and -40dBc integrated-phase-noise 28-to-31 GHz frequency synthesizer based on digital sub-sampling PLL using optimally spaced voltage comparators and background loop-gain optimization," in *IEEE Int. Solid-State Circuits Conf. (ISSCC) Dig. Tech. Papers*, San Francisco, CA, pp. 258-259, Feb. 2019.
- [22] J. Gong et al., "A 10-to-12 GHz 5 mW Charge-Sampling PLL Achieving 50 fsec RMS Jitter, -258.9dB FOM and -65dBc Reference Spur," in *IEEE Radio Frequency Integrated Circuits Symp. Dig.*, pp. 15-18, 2020.
- [23] Z. Zhang, G. Zhu and C. Patrick Yue, "A 0.65-V 12-16-GHz Sub-Sampling PLL With 56.4-fsrms Integrated Jitter and -256.4dB FoM," in *IEEE J. Solid-State Circuits*, vol. 55, no. 6, pp. 1665-1683, June 2020.
- [24] Z. Yang et al., "A 25.4-to-29.5GHz 10.2mW Isolated Sub-Sampling PLL Achieving -252.9dB Jitter-Power FoM and -63dBc Reference Spur," in *IEEE Int. Solid-State Circuits Conf. (ISSCC) Dig. Tech. Papers*, San Francisco, CA, pp. 270-272, Feb. 2019.
- [25] A. Santiccioli et al., "A 66-fs-rms Jitter 12.8-to-15.2-GHz Fractional-N Bang-Bang PLL With Digital Frequency-Error Recovery for Fast Locking," in *IEEE J. Solid-State Circuits*, vol. 55, no. 12, pp. 3349-3361, Dec. 2020.

References [3]

- [26] W. Wu et al., "A 28-nm 75-fsrms Analog Fractional-N Sampling PLL With a Highly Linear DTC Incorporating Background DTC Gain Calibration and Reference Clock Duty Cycle Correction," in *IEEE J. of Solid-State Circuits*, vol. 54, no. 5, pp. 1254-1265, May 2019.
- [27] M. Mercandelli et al., "A 12.5GHz Fractional-N Type-I Sampling PLL Achieving 58fs Integrated Jitter", in *IEEE Int. Solid-State Circuits Conf. (ISSCC) Dig. Tech. Papers*, San Francisco, CA, pp. 274-276, Feb. 2020.
- [28] X. Gao et al., "A 2.7-to-4.3GHz 0.16 ps rms jitter, -246.8 dB FOM digital fractional-N sampling PLL in 28nm CMOS," in *IEEE Int. Solid-State Circuits Conf. (ISSCC) Dig. Tech. Papers*, San Francisco, CA, pp. 174-175, Feb. 2016.
- [29] N. Markulic et al., "A DTC-Based Subsampling PLL Capable of Self-Calibrated Fractional Synthesis and Two-Point Modulation," in *IEEE J. Solid-State Circuits*, vol. 51, no. 12, pp. 3078-3092, Dec. 2016.
- [30] L. Bertulesi et al., "A 30-GHz Digital Sub-Sampling Fractional-N PLL With -238.6-dB Jitter-Power Figure of Merit in 65-nm LP CMOS," in *IEEE J. of Solid-State Circuits*, vol. 54, no. 12, pp. 3493-3502, Dec. 2019.
- [31] W. Wu et al., "A 14nm Analog Sampling Fractional-N PLL with a Digital-to-Time Converter Range-Reduction Technique Achieving 80fs Integrated Jitter and 93fs at Near-Integer Channels," in *IEEE Int. Solid-State Circuits Conf. (ISSCC) Dig. Tech. Papers*, San Francisco, CA, pp. 444-446, Feb. 2021.
- [32] M. B. Dayanik, N. Collins and M. P. Flynn, "A 28.5-33.5 GHz fractional-N PLL using a 3rd order noise shaping time-to-digital converter with 176 fs resolution ", in *Proc. 40th European Solid-State Circuits Conf. (ESSCIRC)*, pp. 376-379, Sep. 2015.
- [33] W. Wu, R. B. Staszewski and J. R. Long, "A 56.4-to-63.4 GHz multi-rate all-digital fractional-N PLL for FMCW radar applications in 65 nm CMOS", in *IEEE J. Solid-State Circuits*, vol. 49, no. 5, pp. 1081-1096, May 2014.
- [34] Y.-L. Hsueh et al., "A 0.29mm² frequency synthesizer in 40nm CMOS with 0.19psrms jitter and <-100dBc reference spur for 802.11ac," in *IEEE Int. Solid-State Circuits Conf. (ISSCC) Dig. Tech. Papers*, San Francisco, CA, pp. 472-474, Feb. 2014.
- [35] Z. Zong et al., "A Low-Noise Fractional-N Digital Frequency Synthesizer With Implicit Frequency Tripling for mm-Wave Applications," in *IEEE J. of Solid-State Circuits*, vol. 54, no. 3, pp. 755-767, March 2019.
- [36] F. Song et al., "A Fractional-N Synthesizer with 110fsrms Jitter and a Reference Quadrupler for Wideband 802.11ax," in *IEEE Int. Solid-State Circuits Conf. (ISSCC) Dig. Tech. Papers*, San Francisco, CA, pp. 264-266, Feb. 2019.
- [37] Y. Lim, et al., "A 170MHz-lock-in-range and -253dB-FoMjitter, 12-to-14.5GHz subsampling PLL with a 150μW frequency-disturbance-correcting loop using a low-power unevenly spaced edge generator," in *IEEE Int. Solid-State Circuits Conf. (ISSCC) Dig. Tech. Papers*, San Francisco, CA, pp. 280-281, Feb. 2020.

References [4]

- [38] W. El-Halwagy et al., "A 28GHz quadrature fractional-N synthesizer for 5G mobile communication with less than 100fs jitter in 65nm CMOS," in Proc. of IEEE Radio Frequency Integrated Circuits Symposium (RFIC), pp. 118-121, June 2016.
- [39] Yoon et al., "A -31dBc integrated-phase-noise 29GHz fractional-N frequency synthesizer supporting multiple frequency bands for backward-compatible 5G using a frequency doubler and injection-locked frequency multipliers," in IEEE Int. Solid-State Circuits Conf. (ISSCC) Dig. Tech. Papers, San Francisco, CA, pp. 366-368, Feb. 2018.
- [40] W. Wu et al., "A 14-nm Low-Cost IF Transceiver IC with Low-Jitter LO and Flexible Calibration Architecture for 5G FR2 Mobile Applications," 2023 IEEE Radio Frequency Integrated Circuits Symposium (RFIC), San Diego, CA, USA, 2023, pp. 277-280.
- [41] S. Hu et al., "A 15.6-GHz Quad-Core VCO with Extended Circular Coil Topology for Both Main and Tail Inductors in 8-nm FinFET Process," 2023 IEEE Radio Frequency Integrated Circuits Symposium (RFIC), San Diego, CA, USA, 2023, pp. 201-204.
- [42] P. T. Renukaswamy et al., "4.1 A 16GHz, 41kHzrms Frequency Error, Background-Calibrated, Duty-Cycled FMCW Charge-Pump PLL," 2023 IEEE International Solid-State Circuits Conference (ISSCC), San Francisco, CA, USA, 2023, pp. 74-76.
- [44] M. Rossoni et al., "10.1 An 8.75GHz Fractional-N Digital PLL with a Reverse-Concavity Variable-Slope DTC Achieving 57.3fsrms Integrated Jitter and -252.4dB FoM," 2024 IEEE International Solid-State Circuits Conference (ISSCC), San Francisco, CA, USA, 2024, pp. 188-190
- [45] D. Xu et al., "10.3 A 7GHz Digital PLL with Cascaded Fractional Divider and Pseudo-Differential DTC Achieving -62.1dBc Fractional Spur and 143.7fs Integrated Jitter," 2024 IEEE International Solid-State Circuits Conference (ISSCC), San Francisco, CA, USA, 2024, pp. 192-194.